

1. Impact of Sizing on Performance

Design and implement an inverter such that $V_M = V_{DD}/2$ using TSMC 180 nm technology.

- Investigate the impact of scaling factor $S > 1$ on the performance of inverter in (i) no external load, and (ii) $C_L = 20pF$ conditions. Tabulate your results.
- What is the impact of increasing W_p or W_n on t_{pHL} and t_{pLH} ? Substantiate your answer by performing simulations and tabulating results.


2. Ring Oscillator

Simulate the transient response of a 7 stage ring oscillator circuit by cascading unit inverters.

- Plot the time response over 10 periods and calculate the frequency of oscillation
- Estimate the propagation delay of the circuit and compare with result in 1(a).
- What is the frequency of oscillation when the inverters are sized up by a factor 'S'? How does the sizing impact the power consumption?
- Suggest a modification to ring oscillator circuit so that a control signal can be used to turn the oscillator *on/off*.

3. Sizing of Inverters

In order to drive a large capacitance ($C_L = 20pF$) from a minimum size gate (with input capacitance $C_i = 10fF$), you decide to introduce a two-staged buffer as shown in Figure 1. Assume that the propagation delay of a minimum size inverter is 70 ps. Also assume that the input capacitance of a gate is proportional to its size.

 **Figure 1**

- Determine the sizing of the two additional buffer stages that will minimize the propagation delay.
- If you could add any number of stages to achieve the minimum delay, how many stages would you insert? What is the propagation delay in this case?
- Describe the advantages and disadvantages of the methods shown in (a) and (b).
- Determine a closed form expression for the power consumption in the circuit. Consider only gate capacitances in your analysis. What is the power consumption for a supply voltage of 2.5V?

4. CMOS Logic

Design a complex CMOS logic gate that implements the function

$$f(A; B; C; D) = \overline{A.(B.(C + D) + C.D)}$$

How do you size the gate to improve it's performance?

5. A particular technology has the following parameters: $V_{th,n} = 0.2 \text{ V}$ and $|V_{th,p}| = 0.3 \text{ V}$, $R_n = 2 \text{ k}\Omega * \mu\text{m}$, $R_p = 3 \text{ k}\Omega * \mu\text{m}$ at $V_{DD} = 1 \text{ V}$. Draw the VTC of the gate below with $W_p = W_n = 1 \mu\text{m}$.

 


Figure 2

Optional Questions

You do not need to submit the following questions, but it is highly recommended that you analyze and answer them.

6. Clock Distribution

Consider the H-tree clock distribution network in Fig. 3. The inverter 1 is a minimum sized inverter with input capacitance of 10 fF . Your goal is to minimize the delay between IN and Clk_1 in the given schematic by choosing appropriate sizes of the inverters. You donot need to worry about the delay in Clk_2 , Clk_3 and Clk_4 branches while answering this question. You may assume $\gamma = 1$.

 


Figure 3

- Some inverter sizes may not influence the delay between IN and Clk_1 . Clearly mark those with a symbol 'X' in the picture above.
- Let the size of remaining inverters be S_i for i^{th} inverter. Write down the expression for time delay between IN and Clk_1 .
- Determine the sizes of remaining inverters so that the above delay is minimized subject to the constraints specified.

7. Logical Effort and Gate Sizing

 


Figure 4

- (a) What is the path effort from In to Out?
- (b) What effective fanout/stage(EF) minimizes the delay of this chain of gates?
- (c) Size the gates to minimize the delay from In to Out.

8. Scaling trends in VLSI circuits

- (a) Sketch the variation of t_{pHL} , t_{pLH} , and t_p as a function of PMOS/NMOS transistor size ratio β for the generic $0.25\ \mu\text{m}$ technology.
- (b) Sketch the functional dependence of $t_p(\text{normalized})$ on effective fanout per stage in a inverter chain in Fig. 8(b). Clearly indicate the effective fanout at which optimal delay is achieved. You may consider $\gamma = 1$, and also account for parasitic overheads.