

# ASSIGNMENT-1

-D.Lakshmi Sivani  
EE18BTECH11012

- 1) a) Operating point through ngspice netlist file is

Simulated file and output:

The screenshot shows a terminal window with the following content:

```
File: /home/sivani/A1/Q1a.net                                         Page 1 of 1
*Netlist
Vin 1 0 2.5V
R 1 out 1k
Rs 3 0 100
C out 3 1u

*Control commands
.control
.op
.print V(out)

Fri 09:23
Terminal ▾
sivani@sivani-Inspiron-5558: ~/A1
File Edit View Search Terminal Help
ngspice 1 -> source Q1a.net
Circuit: *netlist
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 1
v(out) = 2.500000e+00
ngspice 1 -> 
```

So,  $V_{out} = 2.5 \text{ V}$

- 1) b) Given  $V_{in} = \sin(\omega t)$  and  $\omega = 100 \text{ Hz}$  and  $\omega = 1\text{M Hz}$

So for the given circuit the phase lags in both case-1 (when  $\omega = 100 \text{ Hz}$ ) and case-2 (when  $\omega = 1\text{M Hz}$ ) are solved as:

1) b)  $V_{in} = \sin(\omega t)$

Case-1:- When

$$\omega = 100 \text{ Hz (f)}$$

$$\frac{V_{out}}{V_{in}} = \frac{j(\frac{1}{j\omega C} + R_s)}{j(\frac{1}{j\omega C} + R + R_s)}$$

$$\frac{V_{out}}{V_{in}} = \frac{1 + j\omega C R_s}{1 + j\omega C (R + R_s)}$$

$$\text{Phase-Lag } (\phi) = \tan^{-1}\left(\frac{R_s \omega C}{1}\right) - \tan^{-1}\left(\frac{(R + R_s) \omega C}{1}\right)$$

$$\phi = \tan^{-1}(R_s \omega C) - \tan^{-1}((R + R_s) \omega C) \quad \text{--- (1)}$$

$$\phi = \tan^{-1}(10^2 \times 2\pi \times 10^2 \times 10^{-6}) - \tan^{-1}(10^2 \times 2\pi \times 10^2 \times 11 \times 10^{-6})$$

$$\phi = \tan^{-1}(2\pi \times 10^2) - \tan^{-1}(2\pi \times 11 \times 10^2)$$

$$\phi = 3.595^\circ - 34.6503^\circ \approx \underline{\underline{31.05^\circ}}$$

Case-2:- When  $\omega = 1 \text{ MHz (f)} \Rightarrow \omega = 2\pi \times 10^6 \text{ rad/s}$

From eq-1,

$$\phi = \tan^{-1}(R_s \omega C) - \tan^{-1}((R + R_s) \omega C)$$

$$\phi = \tan^{-1}(2\pi \times 10^2) - \tan^{-1}(2\pi \times 11 \times 10^2)$$

$$= 89.908^\circ - 89.9917^\circ$$

$$\approx \underline{\underline{0.0837^\circ}}$$

## Simulation results:

In case-1: When  $\omega = 100 \text{ Hz}$

Netlist file:

```

2.30pm - 8pm
File Open ▾ 2.30pm - 8pm
Q1b_1.net x Q1c.net x Q3.net x Q2b.net x Q4a_1.net x
*Title:Transient analysis


*Netlist
Vin 1 0 Dc 0 AC 1 SIN(0V 1V 100Hz 0 0 0)
R 1 out 1k
Rs 3 0 100
C out 3 1u

*Analysis for 50ms, step size 0.01ms
.tran 0.01ms 50ms

*Control commands
.control
 2 op
    run
    plot V(1) V(out)
 0
  .meas TRAN T1 TRIG V(1) VAL=0 CROSS=2 TARG V(1) VAL=0 CROSS=4
  .meas TRAN T2 TRIG V(1) VAL=0 CROSS=2 TARG V(out) VAL=0 CROSS=2
  let Lag = -360*(T2/T1)
  print Lag

.endc
.end

```

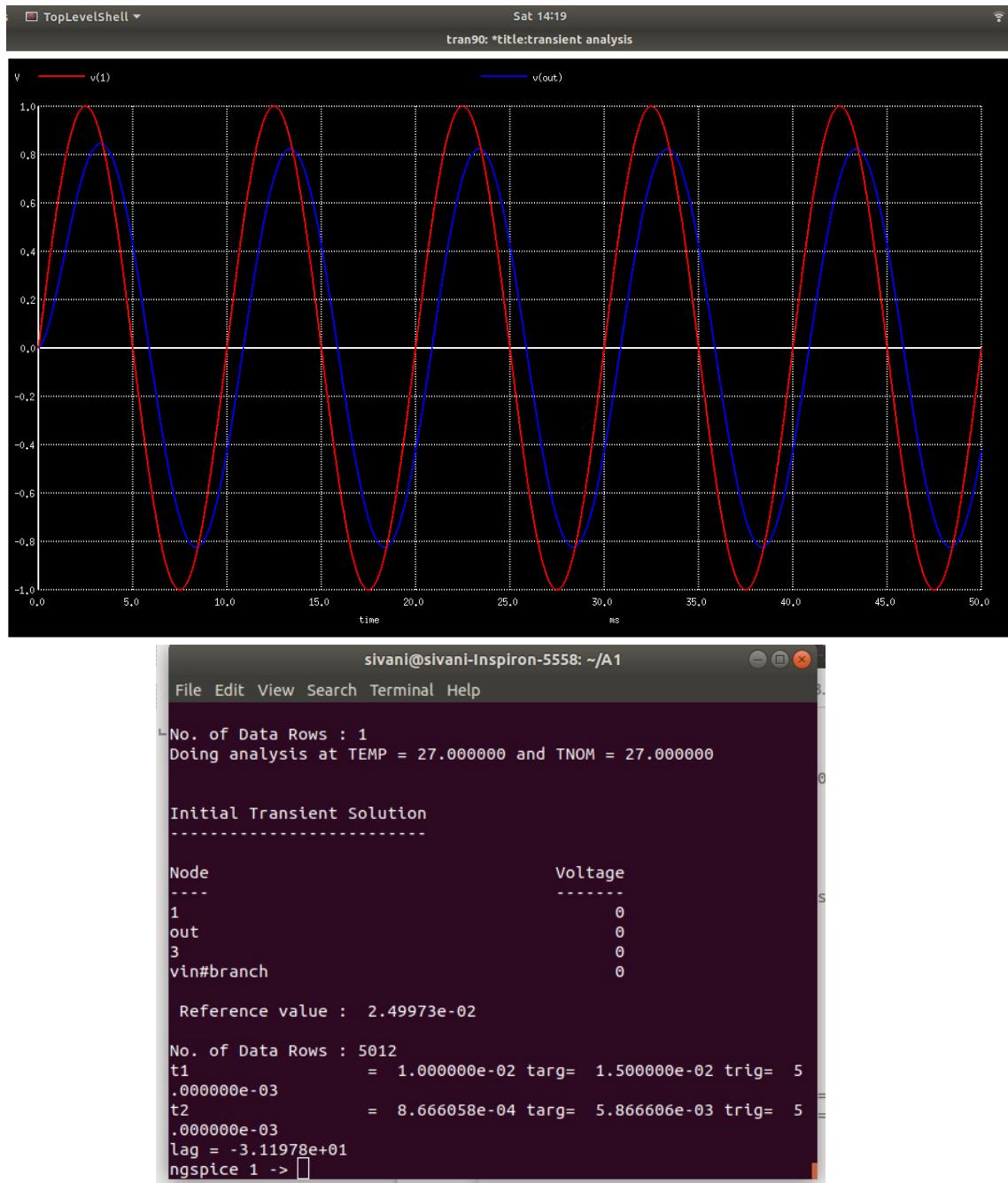

So, The phase-lag obtained in both analytical approach and simulation are same(which is approximately equal to 31.1 degrees).

In case-2: When  $w = 1 \text{ M Hz}$

Netlist file:


```

*Title:Transient analysis
*Netlist
Vin 1 0 Dc 0 AC 1 SIN(0V 1V 1e6Hz 0 0 0)
R 1 out 1k
Rs 3 0 100
C out 3 1u

*Analysis for 5us,step size 2ns
.tran 2n 5us
*Control commands
.control
op
run
plot V(1) V(out)
meas TRAN T1 TRIG V(1) VAL=0 CROSS=2 TARG V(1) VAL=0 CROSS=4
meas TRAN T2 TRIG V(1) VAL=0 CROSS=2 TARG V(out) VAL=0 CROSS=2
let Lag = -360*(T2/T1)
print Lag

.endc
.end

```

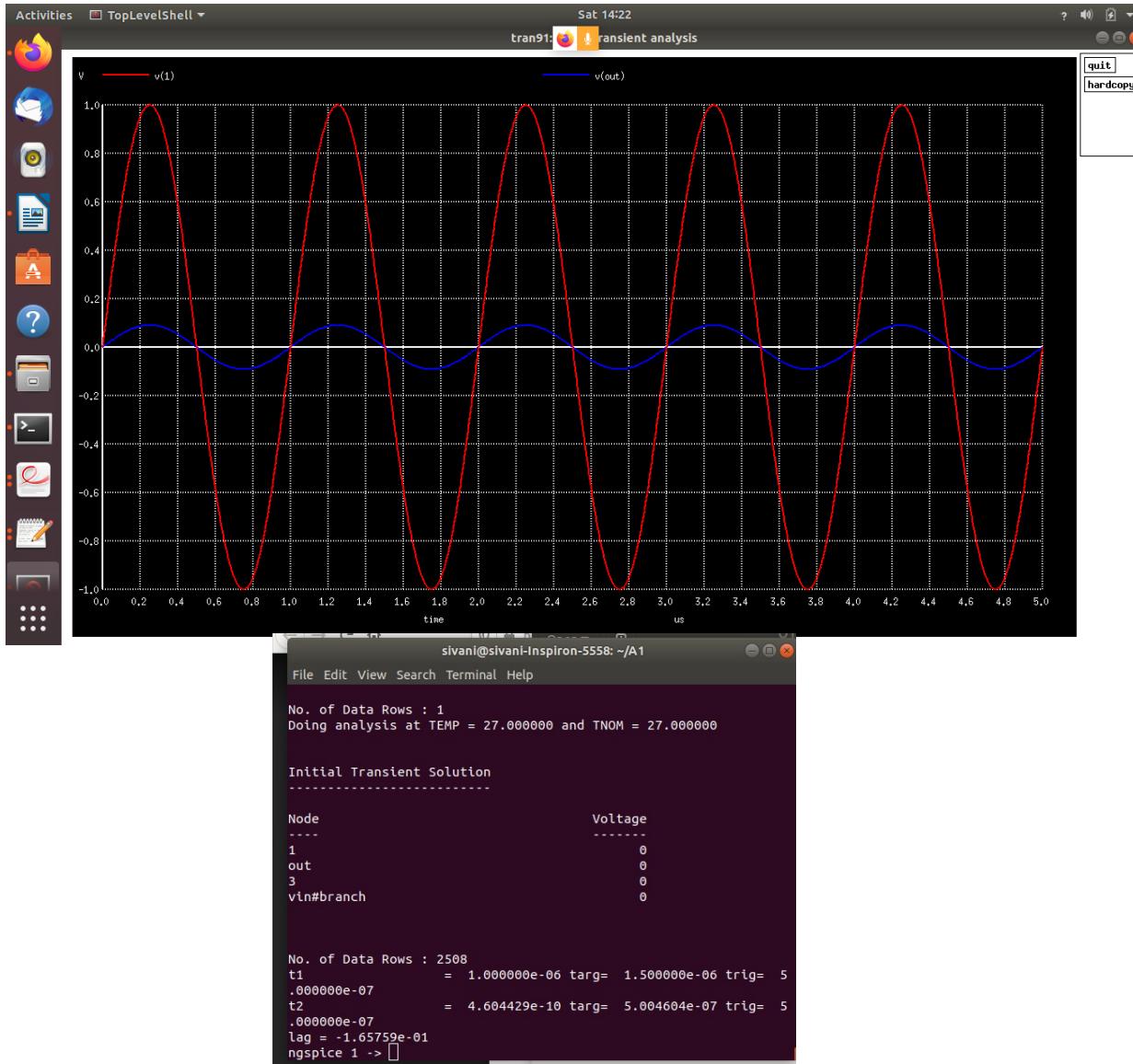

Here also, The phase-lag obtained in both analytical approach and simulation are approximately around 0 degrees.

1) c) Amplitude and Phase transfer characteristics are observed in this way using ngspice simulation:

```


*Title:AC analysis
*Netlist
Vin 1 0 Dc 0 AC 1 SIN(0V 1V 100Hz 0 0 0)
R 1 out 1k
RS 3 0 100
C out 3 1u

*AC analysis for 1 Hz to 1MHz, 10 points per decade
.ac dec 10 1 1Meg
.control
.run


*Magnitude dB plot for v(out) on log scale
plot vdb(out) xlog
*Phase degrees plot for v(out) on log scale
plot {57.29*vp(out)} xlog
meas AC f_3db FIND frequency WHEN Vdb(out)=-3db
let phase = {57.29*vp(out)}
meas AC Phase_lag FIND phase WHEN frequency = f_3db
.endc
.end

```

## Amplitude Characteristics:

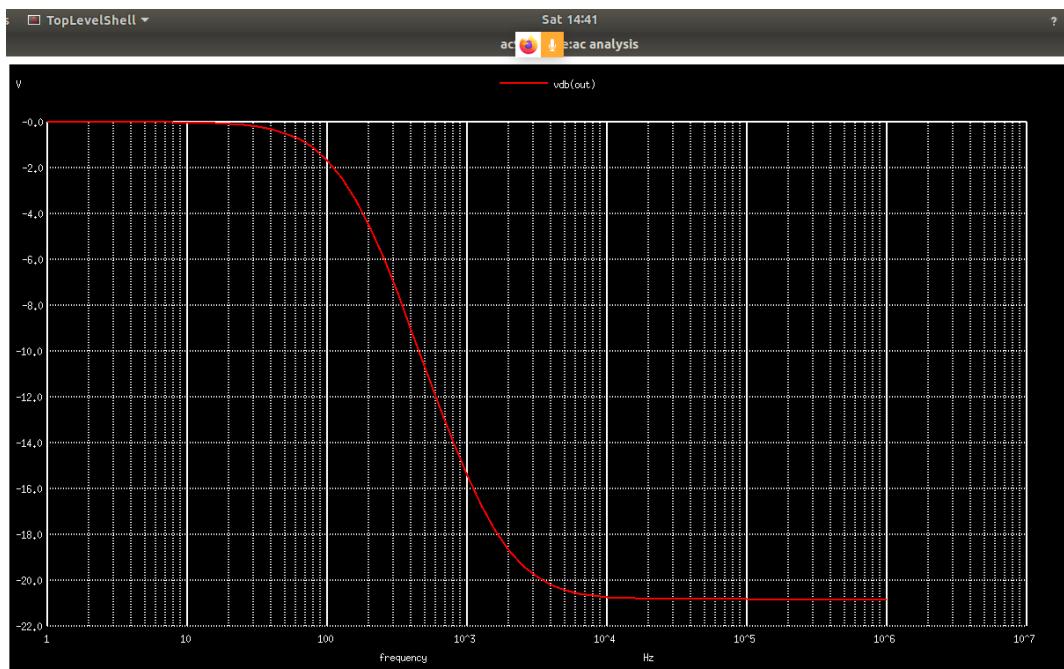

## Phase transfer Characteristics:

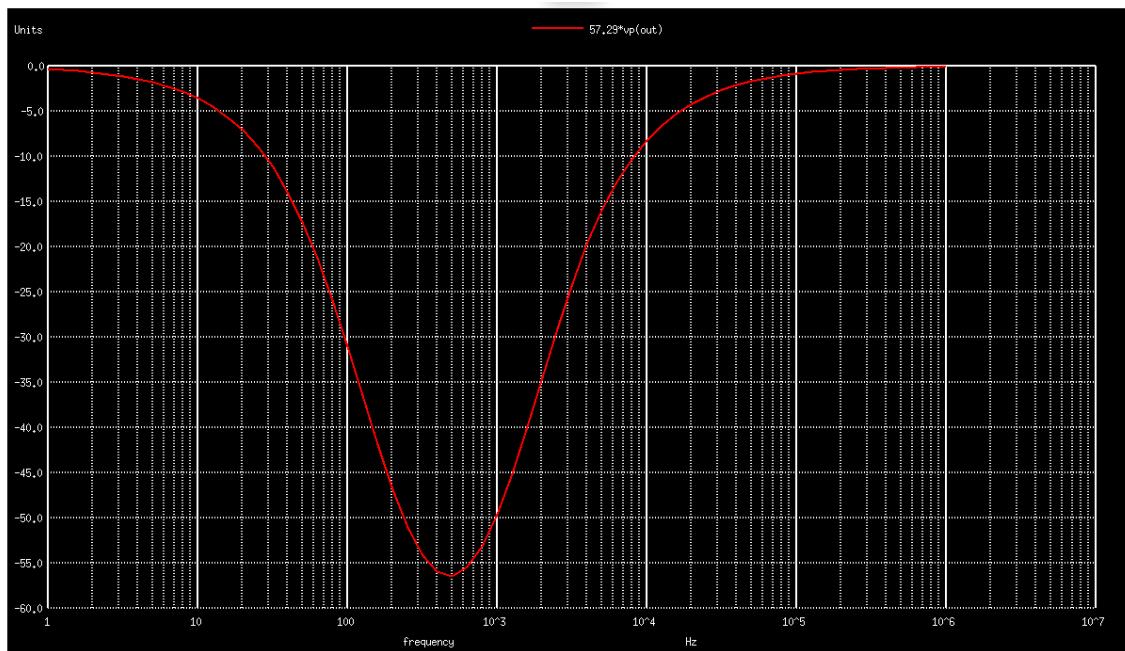

```
sivani@sivani-Inspiron-5558: ~/A1
File Edit View Search Terminal Help
out          0
└ 3          0
vin#branch   0

No. of Data Rows : 2508
t1              = 1.000000e-06 targ= 1.500000e-06 trig= 5
.000000e-07
t2              = 4.604429e-10 targ= 5.004604e-07 trig= 5
.000000e-07
lag = -1.65759e-01
ngspice 1 -> source Q1c.net

Circuit: *title:ac analysis

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 61
f_3db           = 1.455510e+02
phase_lag       = -3.976622e+01
ngspice 1 -> 
```

From the simulation results, we got 3db frequency = 145.55 Hz and Phase lag = 39.76 degrees.

When we calculated these values in analytical approach then

$$\text{Q.C.) } V_{in} = \sin \omega t$$

Here Transfer function is

$$\frac{V_o}{V_{in}} = \frac{1 + j\omega C R_S}{1 + j\omega C (R + R_S)}$$

$$\text{At } 3\text{dB}, \quad \left| \frac{V_o}{V_{in}} \right| = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \frac{\sqrt{1 + \omega^2 C^2 R_S^2}}{\sqrt{1 + \omega^2 C^2 (R + R_S)^2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \frac{\sqrt{1 + \omega^2 (10^6 \times 10^2)^2}}{\sqrt{1 + \omega^2 (11 \times 10^2 \times 10^6)^2}} = \frac{1}{\sqrt{2}} \quad (\text{Assumed } \pi^2 \approx 10)$$

$$\Rightarrow \frac{\sqrt{10^8 + \omega^2}}{\sqrt{10^8 + 121\omega^2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow 2 \times 10^8 + 2\omega^2 = 10^8 + 121\omega^2$$

$$\Rightarrow 119\omega^2 = 10^8$$

$$\therefore \omega = \frac{10^4}{\sqrt{119}} \Rightarrow f = \frac{10^4}{119} \times \frac{1}{2\pi} \text{ Hz}$$

$$\therefore f \approx 145.5 \text{ Hz}$$


At  $f = 145.5 \text{ Hz}$  phase-lag is i.e., at 3dB

$$\phi = \angle H(j\omega)_{3\text{dB}} = \tan^{-1} \left( \frac{2\pi \times 145.5}{10^4} \right) - \tan^{-1} \left( \frac{2\pi \times 145.5}{10^4} \right)$$

$$\therefore \phi \approx -39.76^\circ$$

Even in analytical approach we got 3db frequency = 145.55 Hz and Phase lag = 39.76 degrees.

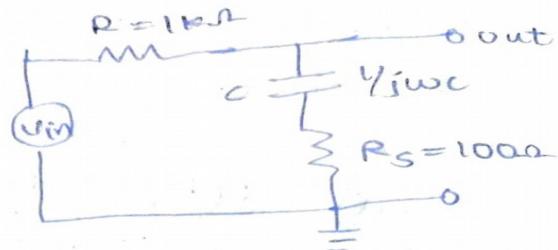So, our results in both approaches are accurate.



2) a) Analytical Calculation for solving  $I_d$  is

2) a) Analytic Calculation:-


Applying KVL for the given circuit then

$$2.5 - (2k)I_D - 0.7 - (2k)I_D = 0$$

$$\Rightarrow (4k)I_D + 1.4 = 2.5$$

$$\Rightarrow (4k)I_D = 1.1$$

$$\therefore I_D = 0.275 \text{ mA}$$

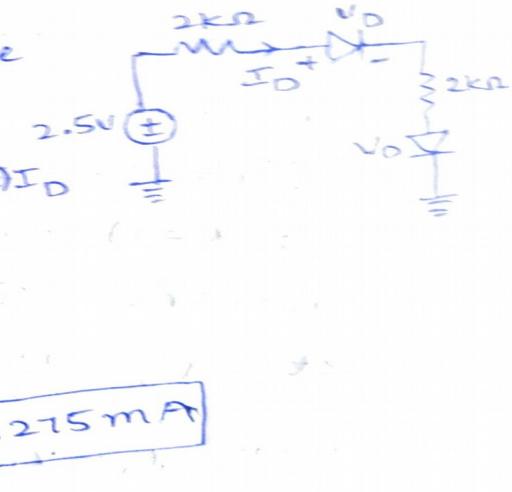

From analytical calculation  $I_D = 0.275 \text{ mA}$ .

2) b) Analytical Calculation for solving  $I_d$  and  $V_d$

2) b) Analytic Calculation:-

Apply KVL

$$(2.5) - (4k)I_D - 2V_D = 0$$

$$(4k)I_D + 2V_D + 2.5 = 0 \quad \text{--- (1)}$$

$$w.k.t n^{(1)} \quad I_D = I_S \left( e^{\frac{qV_D}{nKT}} - 1 \right) \quad \text{Given} \quad I_S = 10^{-14} \text{ A}$$

$$\therefore I_D = 10^{-14} \left( e^{\frac{V_D}{0.0259}} - 1 \right) \quad T = 300 \text{ K}$$

Substitute this in eq-1  $\Rightarrow \frac{KT}{qV} = 0.0259 \text{ eV}$

$$\Rightarrow (4k) \times 10^{-14} \left( e^{\frac{V_D}{0.0259}} - 1 \right) + 2V_D - 2.5 = 0$$

$$\therefore (4 \times 10^{-14}) \left( e^{\frac{V_D}{0.0259}} - 1 \right) + 2V_D - 2.5 = 0$$

$$\text{Let } f(x) = (4 \times 10^{-14}) \left( e^{\frac{x}{0.0259}} - 1 \right) + 2x - 2.5 = 0$$

Solve this equation by any method. For suppose I am solving it in Newton Raphson method.

For that,

$$f(x=0) = -2.5 < 0$$

$$f(x=1) > 0$$

So, there exists one root b/w (0,1).

$$\text{Let } x_0 = \frac{0+1}{2} = 0.5$$

$$\text{then } x_1 = x_0 - \frac{f(x_0)}{f'(x_0)}$$

Iterate this step until  $f(x) = 0$ .

We can solve this in python as shown below. Then we get  $I_D$  as,

$$V_D = 0.6258 V$$

$$\text{So, } I_D = 10^{14} \left( e^{\frac{0.6258}{0.0259}} - 1 \right)^{1/10}$$

$$= 3.115 \times 10^{10} \times 10^{14} A$$

$$I_D = 0.3115 mA$$

Python code for solving the above equation:

```

Toplevel Fri 09:49
*ex.py - /home/sivani/ex.py (3.6.9)*
File Edit Format Run Options Window Help
import numpy as np
import math
import matplotlib.pyplot as plt

def func( x ):
    return (4*pow(10,-11)*(np.exp(x/0.0259)-1))+2*x-2.5

# Derivative of the above function
# which is (4*pow(10,-11)*(np.exp(x/0.0259)))/(0.0259)+2
def derivFunc( x ):
    return (4*pow(10,-11)*(np.exp(x/0.0259)))/(0.0259)+2

# Function to find the root
def newtonRaphson( x ):
    h = func(x) / derivFunc(x)
    while abs(h) >= 0.0001:
        h = func(x)/derivFunc(x)

    # x(i+1) = x(i) - f(x) / f'(x)
    x = x - h

    print("The value of the root is : ",
          "%.4f"% x)

x0=0.5
newtonRaphson(x0)

```

```
Fri 09:49
Python 3.6.9 Shell
File Edit Shell Debug Options Window Help
Python 3.6.9 (default, Oct  8 2020, 12:12:24)
[GCC 8.4.0] on linux
Type "help", "copyright", "credits" or "license()" for more information.
>>> ===== RESTART: /home/sivani/ex.py =====
The value of the root is : 0.6258
>>>
```

So, From analytical calculations  $I_d=0.3115\text{mA}$  and  $V_d=0.6258 \text{ V}$ .  
2) c) Spice simulations for (a) and (b):

For (a):

File: /home/sivani/A1/Q2a.net Page 1 of 1

```
*Title:Solving for Id
*netlist
V1 1 0 2.5v
V2 2 3 0.7v
V3 4 0 0.7v
R1 1 2 2k
R2 3 4 2k

*control
.control
run
op
print -i(V1)
.endc
.end
```

```
sivani@Sivani-Inspiron-5558: ~/A1
File Edit View Search Terminal Help
ngspice 1 -> source Q2a.net
Circuit: *title:solving for id

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

1

No. of Data Rows : 1
-i(v1) = 2.750000e-04
ngspice 1 -> []
```

From spice simulation,we got  $I_d = 0.275 \text{ mA}$  (which is similar to our analytical value)

For (b):

File: /home/sivani/A1/Q2b.net Page 1 of 1

```
*Title:Q2(b)-Solving Id and Vd

*Netlist
V1 1 0 2.5V
R1 1 2 2k
D1 2 3 mydiode
R2 3 4 2k
D2 4 0 mydiode
.MODEL mydiode D (IS=1e-14)

*control
.control
run
op
print -i(V1)
print V(4)
.endc
.end
```

```
sivani@sivani-Inspiron-5558: ~/A1
File Edit View Search Terminal Help
ngspice 1 -> source Q2b.net
Circuit: *title:q2(b)-solving id and vd
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 1
-i(v1) = 3.124924e-04
v(4) = 6.250153e-01
ngspice 1 -> 
```

From spice simulation,we got  $I_d = 0.312 \text{ mA}$  and  $V_d = 0.625 \text{ V}$ (which are similar to our analytical values)

3) Simulation results for output response and Gain of circuit are-

Netlist file:


File: /home/sivani/A1/Q3.net Page 1 of 1

```
*Title:Gain of the circuit

*Netlist
Vin 0 in ac SIN(0V 0.5V 1kHz 0 0 0)
Rin 0 in 1 1K
Rf 1 out 3k
R out 0 1
G1 0 out (0,1) 1e6

*Analysis for 5ms,step size 0.01ms
.tran 0.01ms 5ms
.control
run
meas TRAN Voutmax MAX V(out)
meas TRAN Vinmax MAX V(in)
let Gain = -Voutmax/Vinmax
plot V(out) V(in)
print Gain
.endc
.end
```

## Output response:

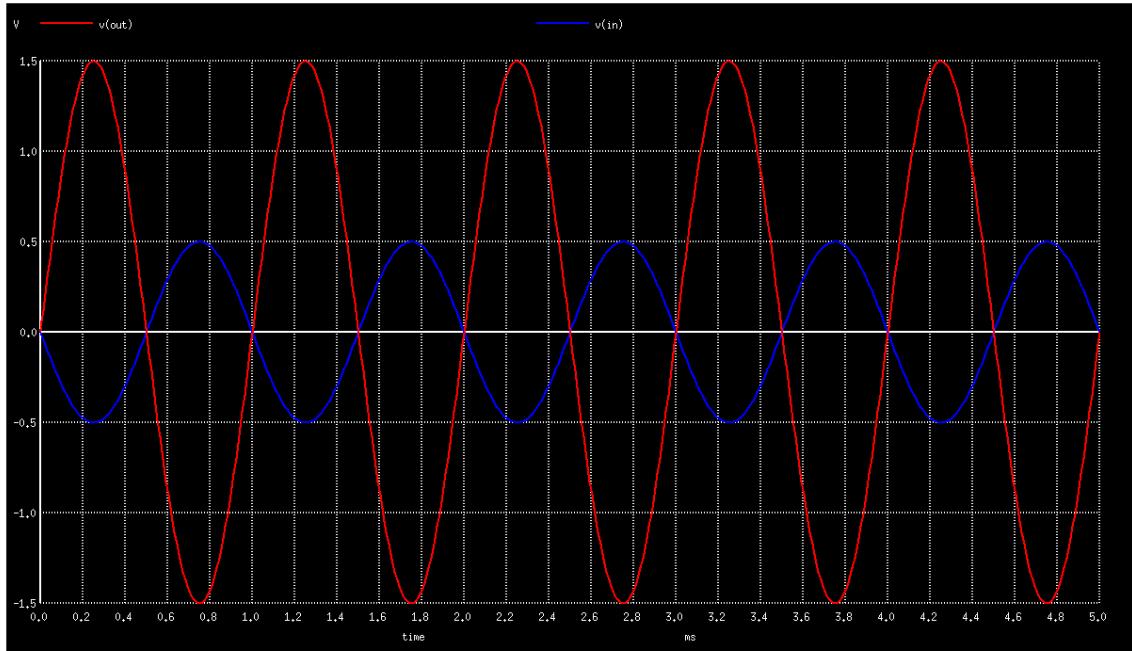

The red wave is output response and the blue one is input voltage.

## Gain of the circuit:

```
sivani@sivani-Inspiron-5558:~/A1
File Edit View Search Terminal Help
*Circuit: *title:gain of the circuit
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Warning: vin: no DC value, transient time 0 value used
Initial Transient Solution
-----
Node          Voltage
-----
in           0
1            0
out          0
vin#branch   0

No. of Data Rows : 508
voutmax       =  1.499762e+00 at=  4.252800e-03
vinmax        =  4.999226e-01 at=  4.752800e-03
gain = -2.99999e+00
ngspice 1 -> □
```

Here, Gain of the circuit is “-3”.

## 4) Mosfet Characteristics

a) ‘Id’ Vs ‘Vds’

## For Short Channel nmos :


Netlist file:

```
*Title:Q4a- NMOS
.include TSMC180.lib
.model nch_tt nmos

*Netlist
*M1 ds gs 0 0 nch_tt W=15u L=10u
M1 ds gs 0 0 nch_tt W=0.27u L=0.18u
V1 ds 0 DC 0
V2 gs 0 DC 1.5V

.control
dc V1 0 1.8 0.01
*plot -i(V1) vs V(ds)
wrdata nmoss2.dat -i(v1) vs v(ds)
print -i(V1) V(ds)
.endc
.end
```

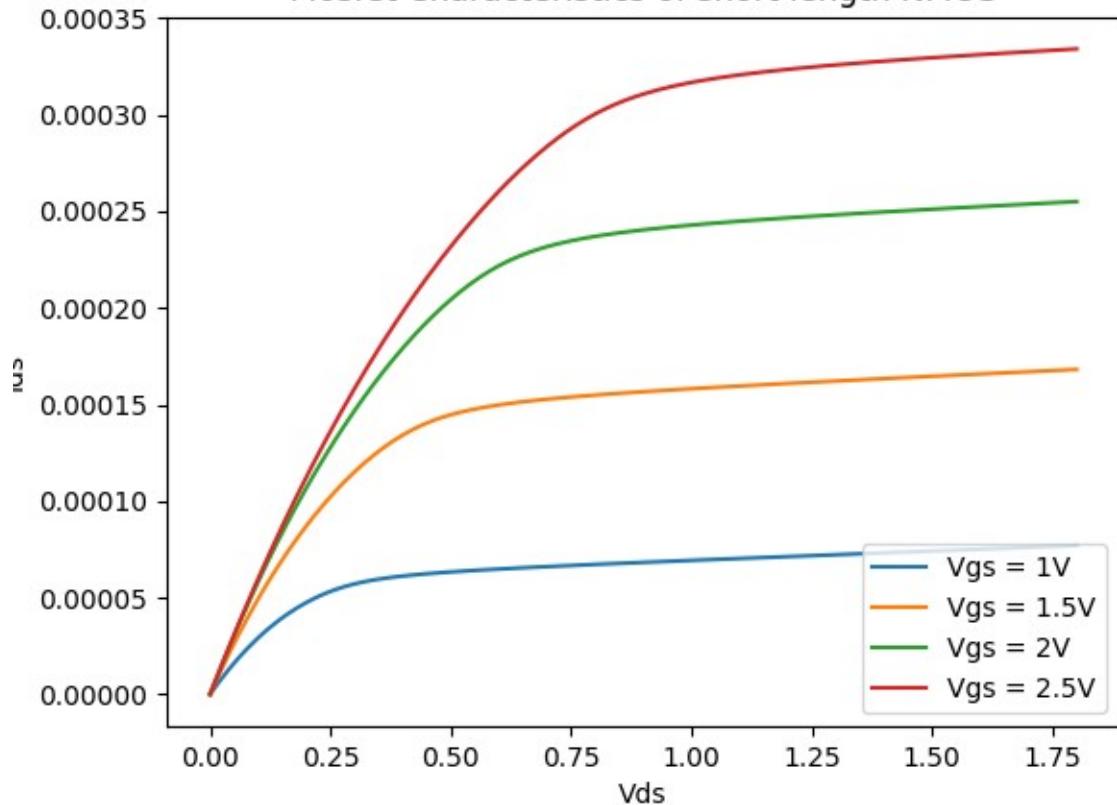Mosfet Characteristics of short length NMOS




## For Long Channel nmos:

Netlist file:

```
*Title:Q4a- NMOS
.include TSMC180.lib
.model nch_tt nmos

*Netlist
M1 ds gs 0 0 nch_tt W=15u L=10u
V1 ds 0 DC 0
V2 gs 0 DC 1.5V

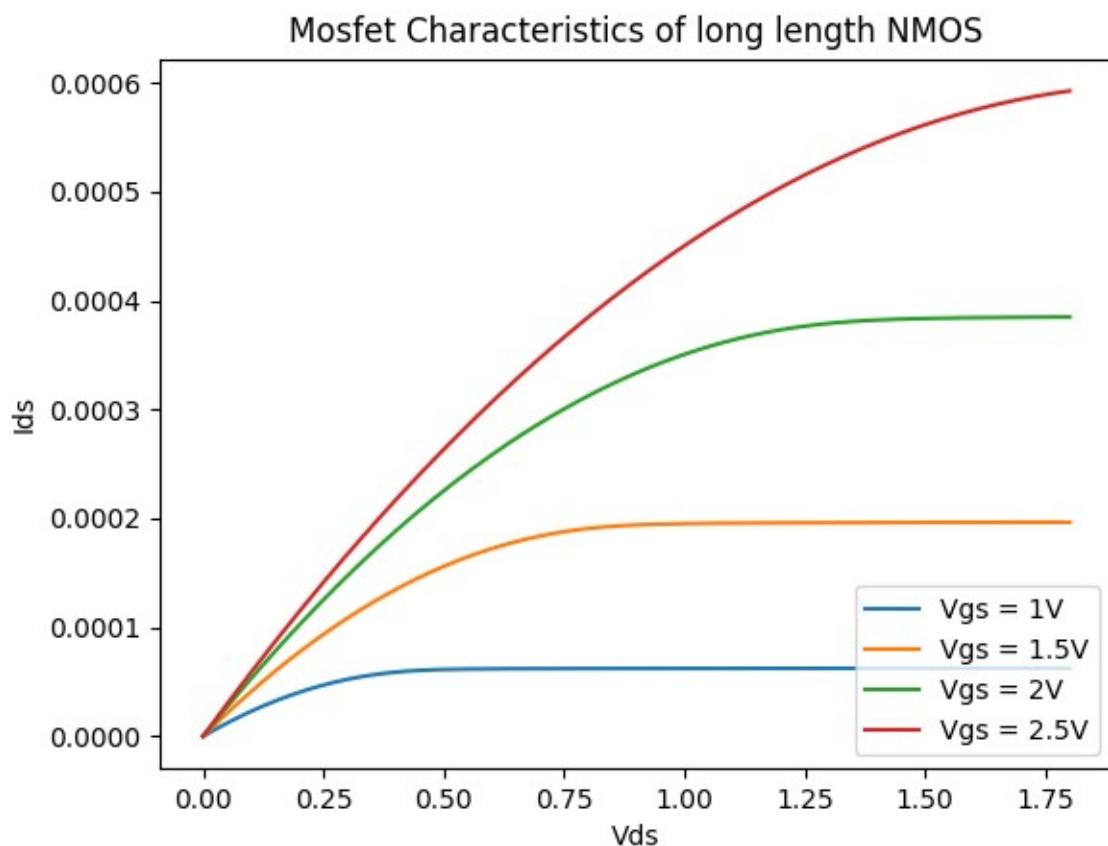.control
dc V1 0 1.8 0.01
*plot -i(V1) vs V(ds)
wrdata nmosl4.dat -i(v1) vs v(ds)
print -i(V1) V(ds)
.endc
.end
```



For Short Channel pmos :


Netlist file:

```
*Title:Q4a- PMOS
.include TSMC180.lib
.model pch_tt pmos
*Netlist
*M1 ds gs 0 0 pch_tt W=15u L=10u
M1 ds gs 0 0 pch_tt W=0.27u L=0.18u
V1 ds 0 DC 0
V2 gs 0 DC -1V

.control
dc V1 0 -1.8 -0.01
*plot -i(V1) vs V(ds)
wrdata pmoss4.dat -i(v1) vs v(ds)
.endc
.end
```

Plain Text ▾ Tab Width: 8 ▾ Ln 11, Col 14 ▾ INS

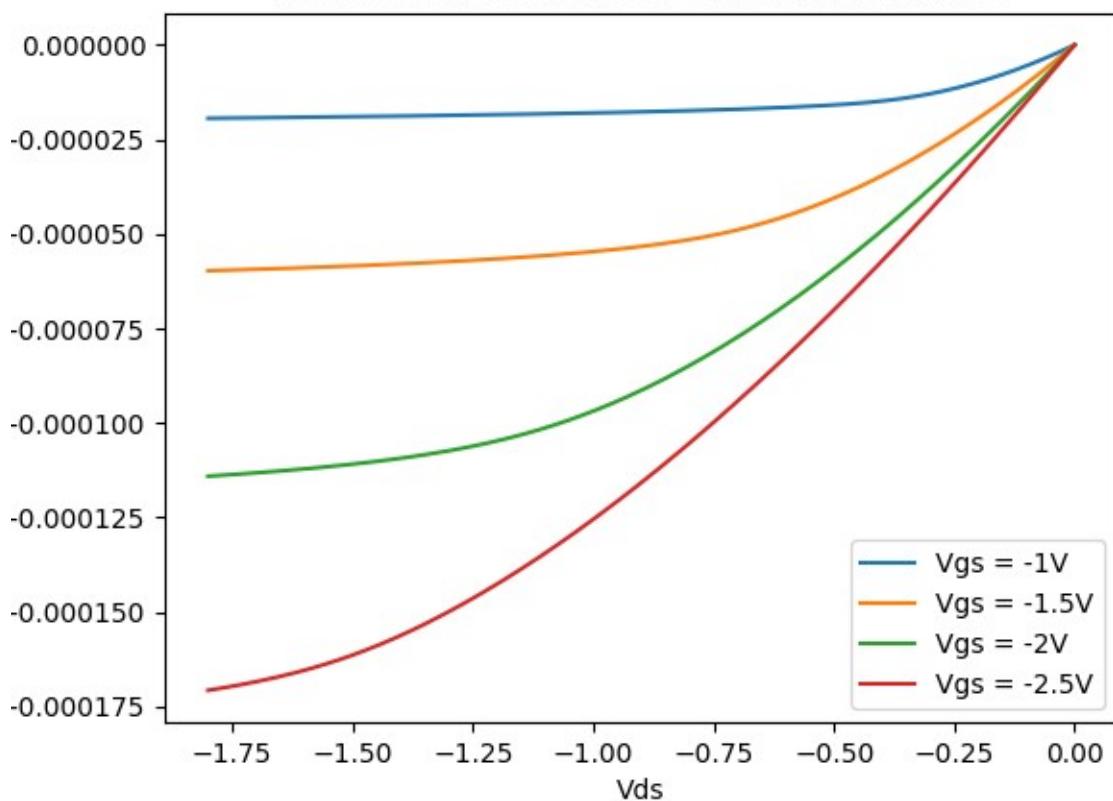
### Mosfet Characteristics of short channel PMOS



For Long Channel pmos :

Netlist file:
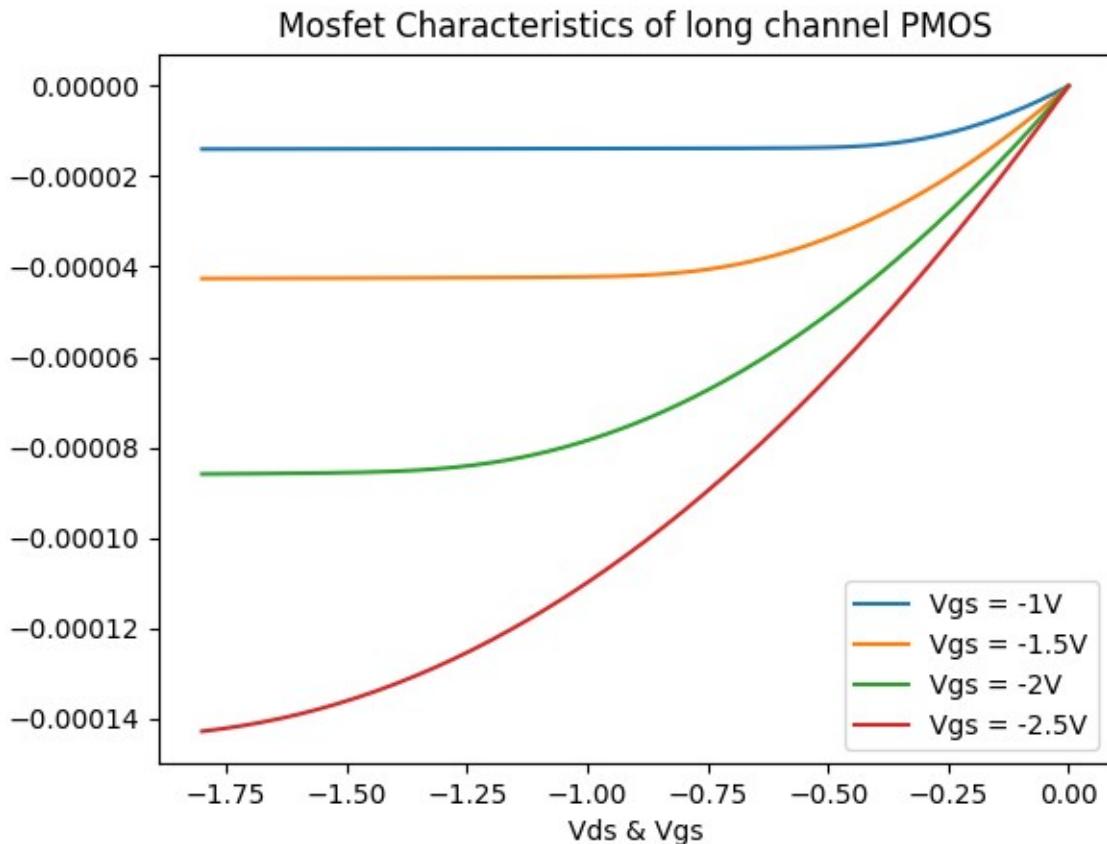
```
*Title:Q4a- PMOS
.include TSMC180.lib
.model pch_tt pmos
*Netlist
M1 ds gs 0 0 pch_tt W=15u L=10u
V1 ds 0 DC 0
V2 gs 0 DC -1V
.control
dc V1 0 -1.8 -0.01
*plot -i(V1) vs V(ds)
wrdata pmosl4.dat -i(v1) vs v(ds)
.endc
.end
```



#### 4) b) Linear and Saturation regions

These regions are identified from ‘Id’ Vs ‘Vgs-Vth’ plot.

We use netlist files for simulating the ‘Id’ vs ‘Vgs’ plot for MOS devices.(just like above (a)).

#### For Long Channel nmos:

Netlist file:

```
*Title:Q4b- NMOS
.include TSMC180.lib
.model nch_tt nmos
*Netlist
M1 ds gs 0 0 nch_tt W=15u L=10u
V1 ds 0 DC 1.8
V2 gs 0 DC 0
.control
dc V2 0 1.8 0.01
*plot -i(V1) vs V(gs)
wrdata plot1.dat -i(v1) vs v(gs)
.endc
.end
```

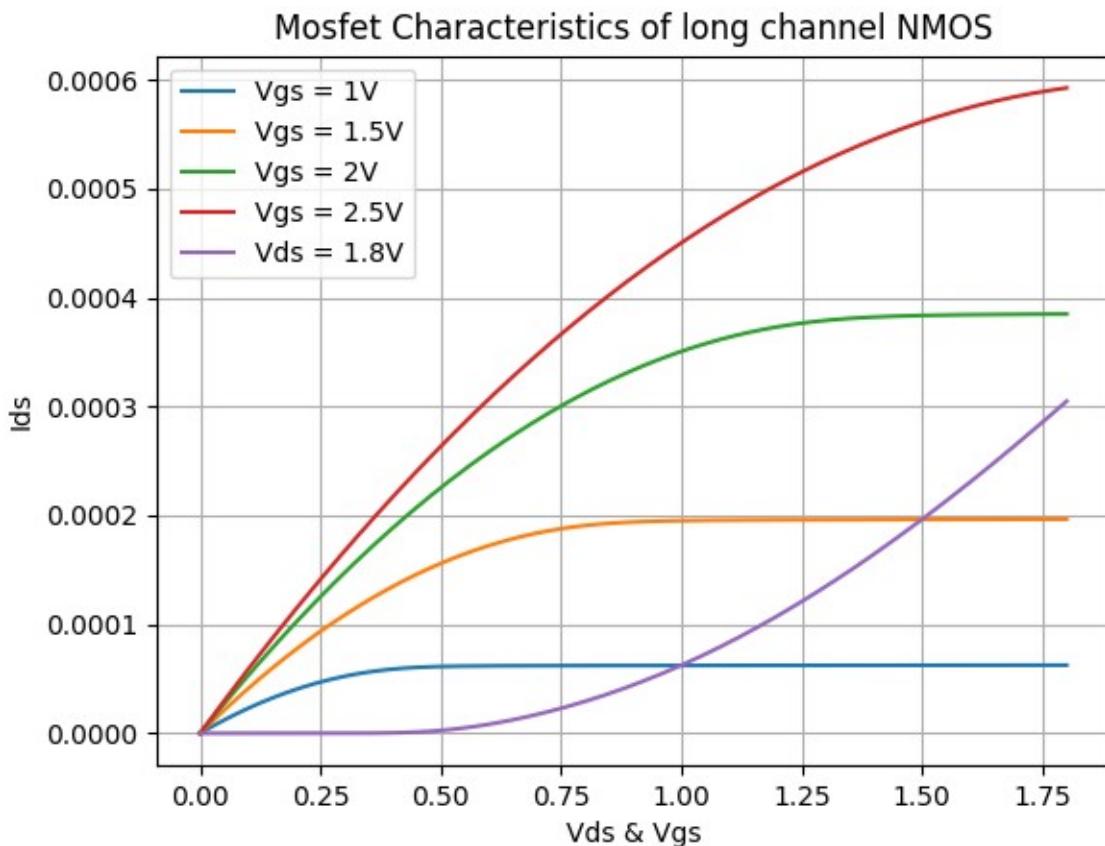


Fig-1

For Short Channel nmos:

Netlist file:

```
*Title:Q4b- NMOS
.include TSMC180.lib
.model nch_tt nmos

*Netlist
M1 ds gs 0 0 nch_tt W=0.27u L=0.18u
V1 ds 0 DC 1.8
V2 gs 0 DC 0

.control
dc V2 0 1.8 0.01

*plot -i(V1) vs V(gs)
wrdata plot2.dat -i(v1) vs v(gs)
.endc
.end
```

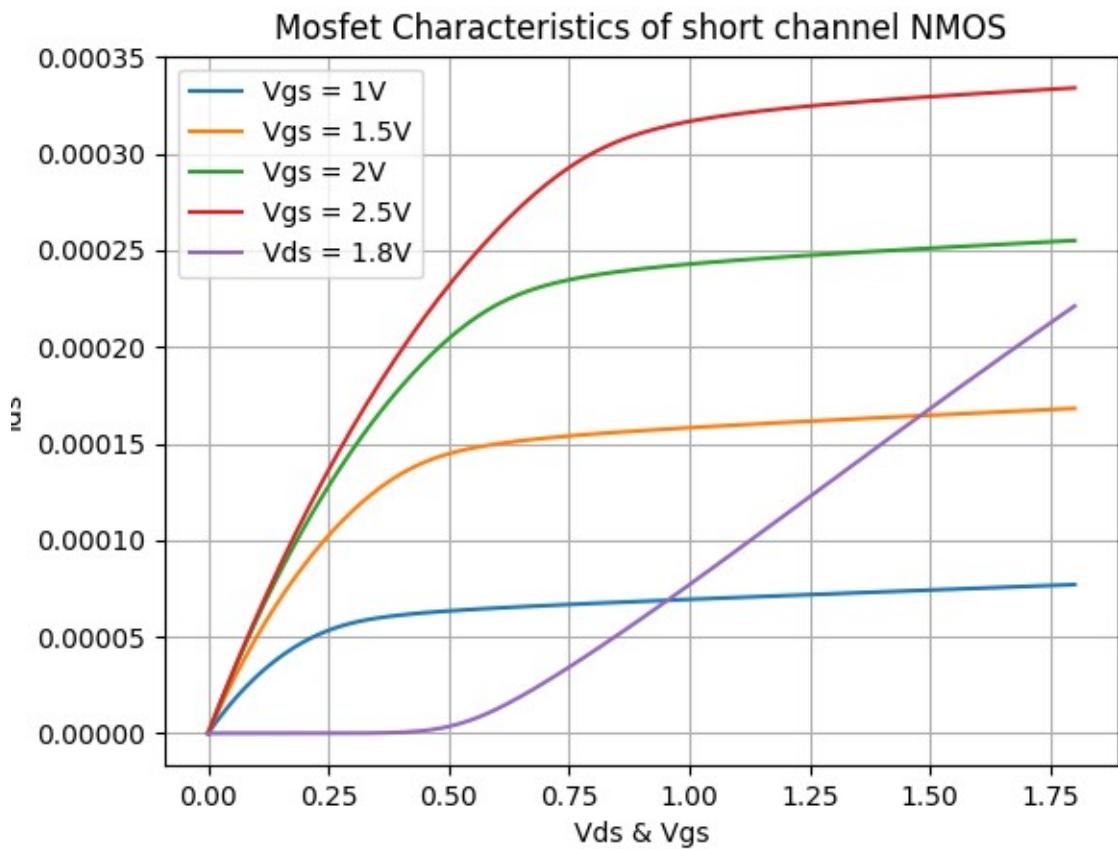


Fig-2

For Short Channel pmos:

Netlist file:

```
*Title:Q4b- PMOS
.include TSMC180.lib
.model pch_tt pmos

*Netlist

M1 ds gs 0 0 pch_tt W=0.27u L=0.18u
V1 ds 0 DC -1.8
V2 gs 0 DC 0

.control
dc V2 0 -1.8 -0.01

*plot -i(V1) vs V(gs)
wrdata plot3.dat -i(v1) vs v(gs)
.endc
.end
```

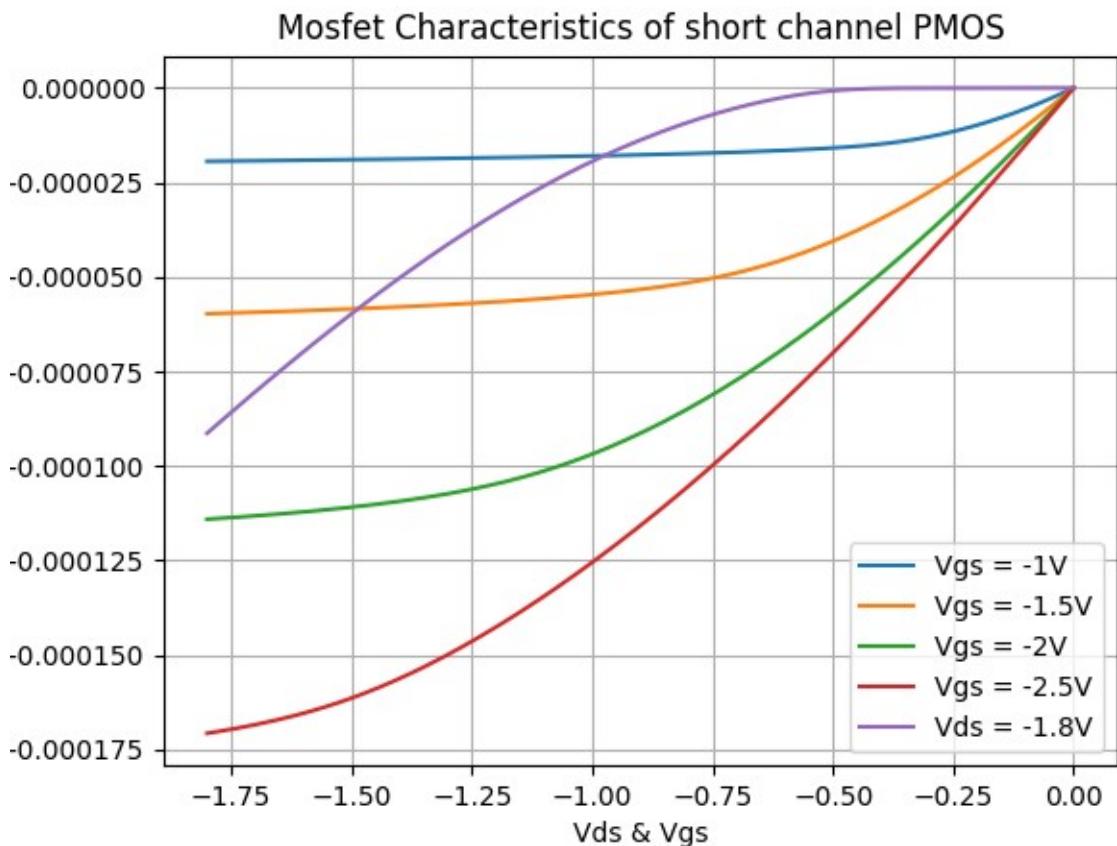


Fig – 3

For Long Channel pmos:

Netlist file:

```
*Title:Q4b- PMOS
.include TSMC180.lib
.model pch_tt pmos

*Netlist

M1 ds gs 0 0 pch_tt W=15u L=10u
V1 ds 0 DC -1.8
V2 gs 0 DC 0

.control
dc V2 0 -1.8 -0.01

*plot -i(V1) vs V(gs)
wrdata plot4.dat -i(v1) vs v(gs)
.endc
.end
```

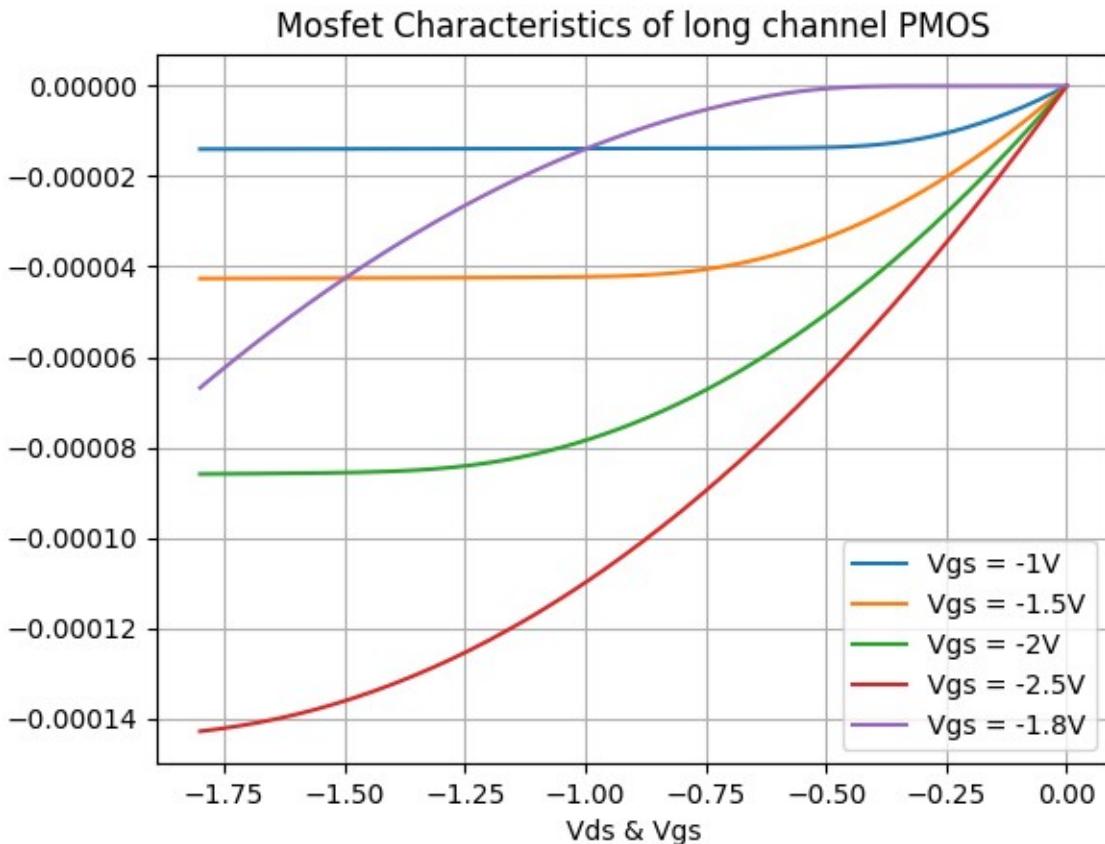


Fig-4

In all these above figures -1,2,3 and 4 :

- The region to the right of ‘ $I_d$ ’ Vs ‘ $V_{gs}-V_{th}$ ’ is **Saturation region** .
- Whereas the region to the left of ‘ $I_d$ ’ Vs ‘ $V_{gs}-V_{th}$ ’ is **Linear region**.

4) c) Small signal output resistance is given by inverse of slope of  $I_d$  Vs  $V_{ds}$  curve in saturation region.

Slope can be calculated by taking two points present in saturation region in the plot.

For example,

Lets take slope of  $I_d$  Vs  $V_{ds}$  plot in short channel nmos when  $V_{gs}=1.5$  V  
[ Take two points in saturation region from simulation attached below ]

$$\text{Slope} = \Delta I / \Delta V = (0.00115 \times 10^{-4}) / (10^{-2})$$

$$= 115 \times 10^{-7}$$

So, small signal output resistance =  $1 / (\text{slope}) = 86956.5 \Omega$

```
sivani@sivani-Inspiron-5558: ~/A1
File Edit View Search Terminal Help
163 1.630000e+00 1.661826e-04 1.630000e+00
164 1.640000e+00 1.662998e-04 1.640000e+00
165 1.650000e+00 1.664168e-04 1.650000e+00
166 1.660000e+00 1.665336e-04 1.660000e+00
167 1.670000e+00 1.666503e-04 1.670000e+00
168 1.680000e+00 1.667669e-04 1.680000e+00
169 1.690000e+00 1.668833e-04 1.690000e+00
170 1.700000e+00 1.669996e-04 1.700000e+00
Index v-sweep -i(v1) v(ds)
-----
171 1.710000e+00 1.671158e-04 1.710000e+00
172 1.720000e+00 1.672318e-04 1.720000e+00
173 1.730000e+00 1.673477e-04 1.730000e+00
174 1.740000e+00 1.674635e-04 1.740000e+00
175 1.750000e+00 1.675792e-04 1.750000e+00
176 1.760000e+00 1.676947e-04 1.760000e+00
177 1.770000e+00 1.678101e-04 1.770000e+00
178 1.780000e+00 1.679255e-04 1.780000e+00
179 1.790000e+00 1.680407e-04 1.790000e+00
180 1.800000e+00 1.681558e-04 1.800000e+00
ngspice 1 ->[]
```

Similarly, small signal output resistance in other three cases(i.e., Long channel nmos, short and long channel pmos) are calculated.

They are obtained as-(When  $V_{gs} = 1.5 \text{ V}$ )

- In long channel nmos,  
slope =  $7.104 \times 10^{-7}$

So, Small signal output resistance =  $1.4 \text{ M}\Omega$

- In short channel pmos,

slope =  $2.81 \times 10^{-6}$

So, Small signal output resistance =  $355871 \Omega$

- In long channel pmos,  
slope =  $2.127 \times 10^{-7}$

So, Small signal output resistance =  $4.7 \text{ M}\Omega$

4) d) Id – Vg characteristics on a log-linear scale:

For short channel nmos:

Netlist file:

```
*Title:Short channel NMOS
.include TSMC180.lib
.model nch_tt nmos

*Netlist
*M1 ds gs 0 0 nch_tt W=15u L=10u
M1 ds gs 0 0 nch_tt W=0.27u L=0.18u
V1 ds 0 DC 1.8
V2 gs 0 DC 0

.control
dc V2 0 1.8 0.01
plot log10(-i(V1)) vs v(gs)

.endc
.end
```


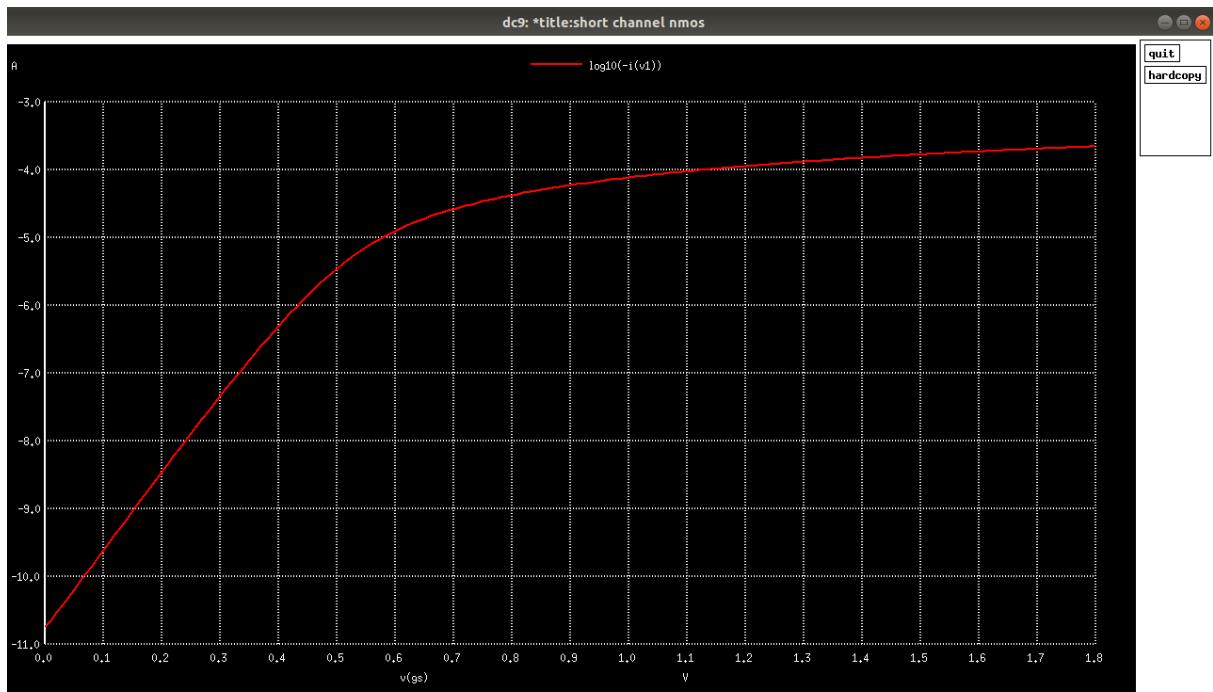


Fig -1: Id-Vg characteristics of short channel nmos

Subthreshold slope:It is defined as the slope of Id-Vg curve in the region until Vg reaches  $V_t$ .

Considering two points in this region  
(110,-9.5) and (240,-8)
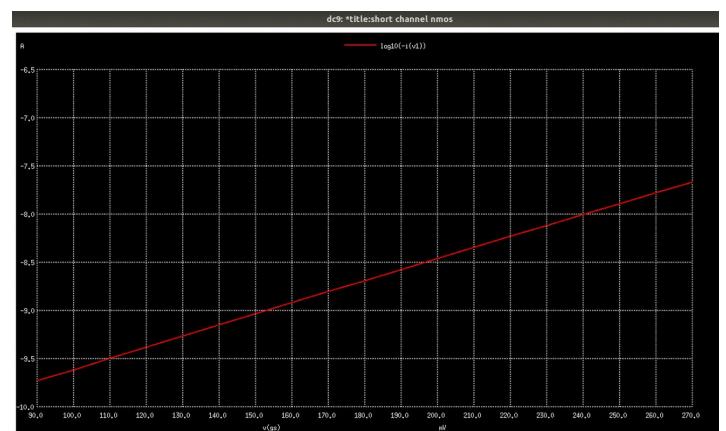
$$\text{Sub threshold slope} = \Delta V / \Delta I = 130 / 1.5$$



So, Sub threshold slope = 86.67 mV/decade

For Long channel nmos:

Netlist file:

```
*Title:Long channel NMOS
.include TSMC180.lib
.model nch_tt nmos

*Netlist

M1 ds gs 0 0 nch_tt W=15u L=10u
*M1 ds gs 0 0 nch_tt W=0.27u L=0.18u
V1 ds 0 DC 1.8
V2 gs 0 DC 0

.control
dc V2 0 1.8 0.01
plot log10(-i(V1)) vs v(gs)
.endc
.end
```

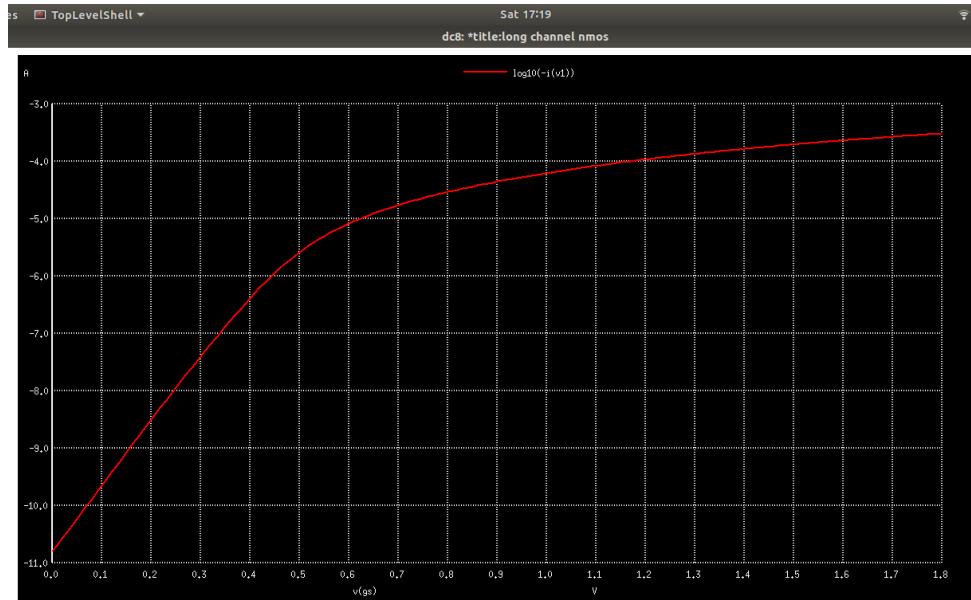



Fig -2: Id-Vg characteristics of long channel nmos

Considering two points in this region  
(70,-10) and (140,-9.2)

Sub threshold slope =  $\Delta V / \Delta I$

$$= 70 / 0.8$$

$$= 87.5 \text{ mV/decade}$$

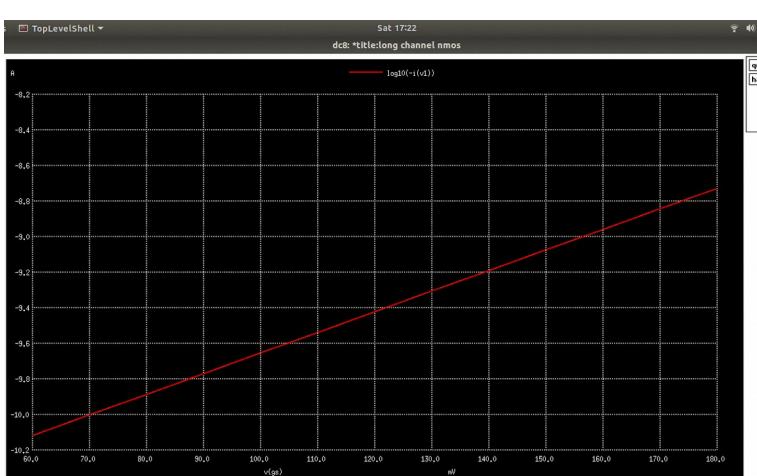

So, subthreshold slope is 87.5 mV/decade.

For short channel pmos:

Netlist file:

```
*Title:Short channel PMOS
.include TSMC180.lib
.model pch_tt pmos

*Netlist
*M1 ds gs 0 0 pch_tt W=15u L=10u
M1 ds gs 0 0 pch_tt W=0.27u L=0.18u
V1 ds 0 DC -1.8
V2 gs 0 DC 0

.control
dc V2 0 -1.8 -0.01
plot log10(abs(-i(V1))) vs V(gs)
.endc
.end
```

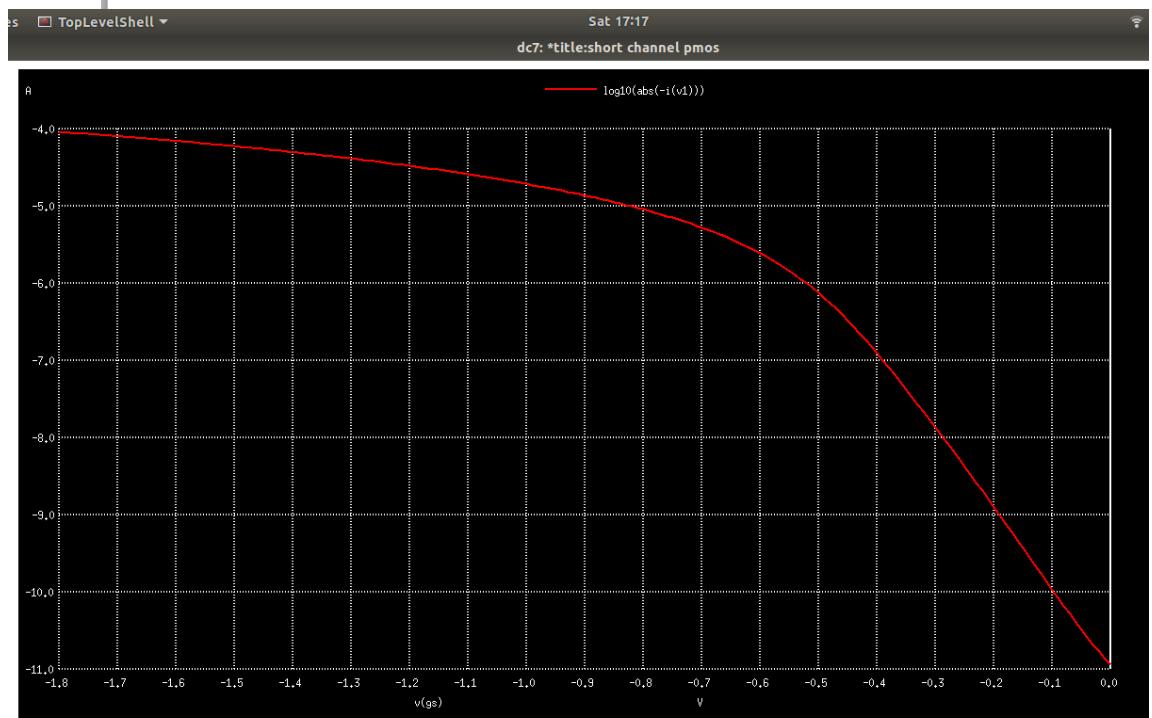



Fig -3: Id-Vg characteristics of short channel pmos

Considering two points in this region  
(-210,-8.8) and (-190,-9) then

Sub threshold slope =  $\Delta V / \Delta I$

$$= 20 / -0.2$$

$$= -100 \text{ mV/decade}$$

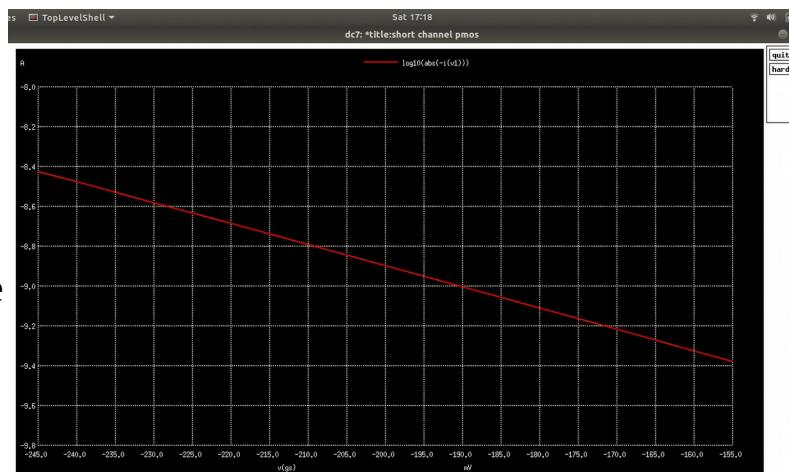

So, sub threshold slope is -100 mV/dec.

For long channel pmos:

Netlist file:

```
*Title:Long channel PMOS
.include TSMC180.lib
.model pch_tt pmos

*Netlist
M1 ds gs 0 0 pch_tt W=15u L=10u
*M1 ds gs 0 0 pch_tt W=0.27u L=0.18u
V1 ds 0 DC -1.8
V2 gs 0 DC 0

.control
dc V2 0 -1.8 -0.01
plot log10(abs(-i(v1))) vs v(gs)
.endc
.end
```

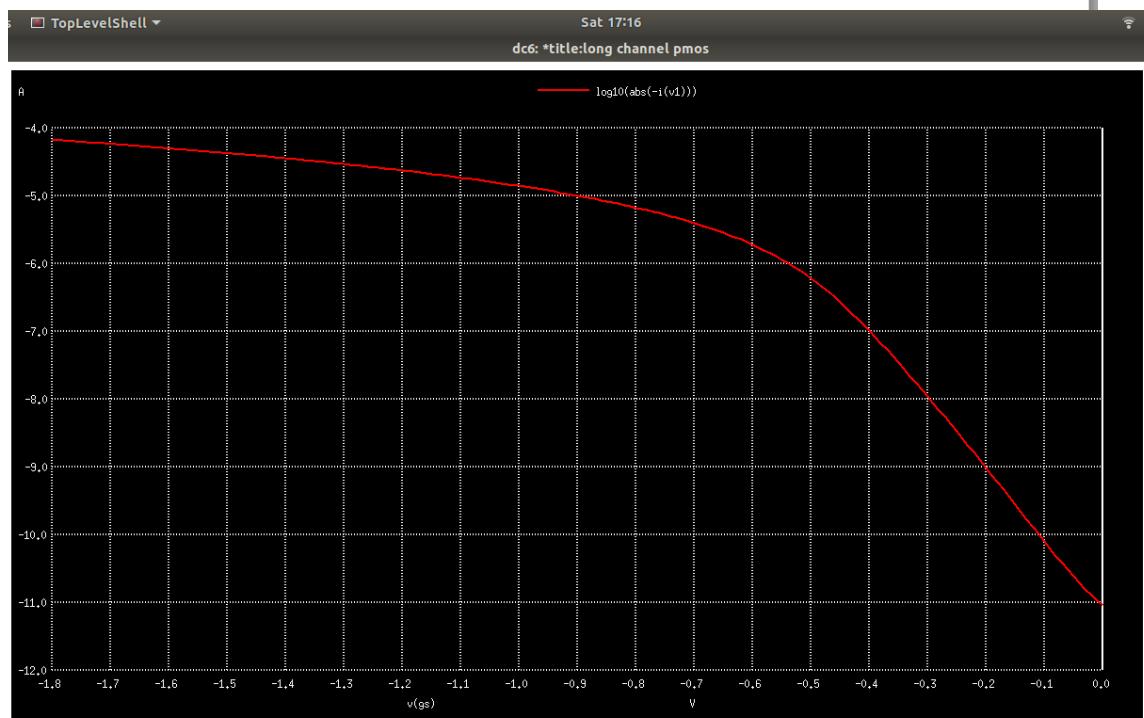



Fig -4: Id-Vg characteristics of long channel pmos

Considering two points in this region  
 $(-220, -8.8)$  and  $(-210, -8.9)$  then  
 Sub threshold slope =  $\Delta V / \Delta I$

$$= 10 / -0.1$$

$$= -100 \text{ mV/decade}$$

So, sub threshold slope is -100 mV/dec.

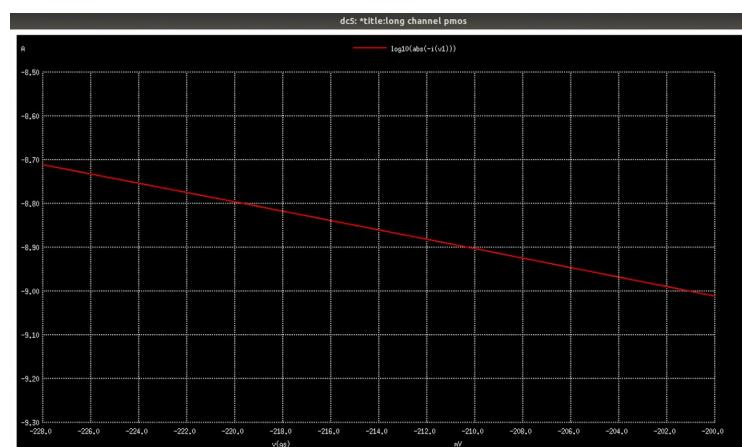

## 5) Propagation Delay

Given first order RC circuit having propagation delay for an ideal step input( $t_r, in = 0$ ) is  $tp = 0.69RC$ . Further, the output rise time  $t_r = 2.2RC$ .

To verify this circuit satisfying given relation I am choosing R and C values as  $R = 1k \Omega$  and  $C = 1pF$  then


Propagation delay ( $tp$ ) should become 0.69 ns and Rise time should become 2.2 ns.

5) a) So, For this we shall verify simulating the circuit in ngspice.

Netlist file:

```
**Propagation delay*
V1 in 0 PULSE(0 1 0 0 0)
R1 in out 1k
C1 out 0 1p
.tran 0.01ns 15n

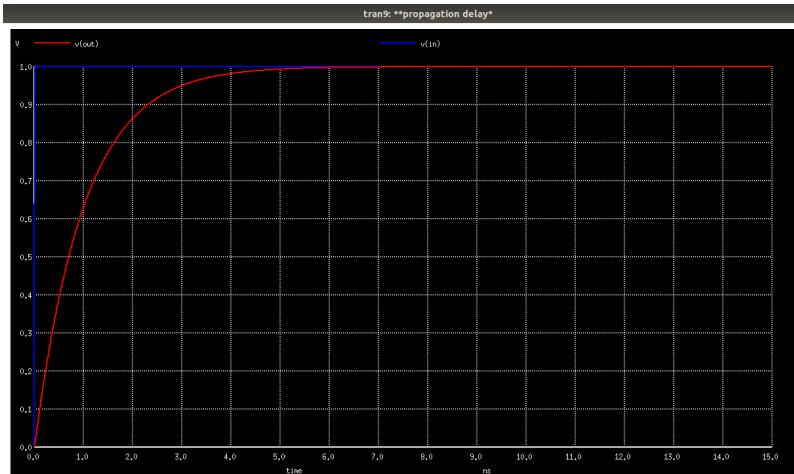.control
run
plot V(out) V(in)
meas tran peak MAX V(out)
let vp = peak/2
imeas tran Tp find time when V(out)=vp cross=1
print Tp
let v2 = 0.1*peak
imeas tran T2 find time when V(out)=v2
imeas tran T3 find time when V(out)=v3
let tr= T3-T2
print tr
.endc
.end
```



Output and Input wave forms

sivani@sivani-Inspiron-5558: ~/A1  
File Edit View Search Terminal Help  
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000  
Warning: v1: no DC value, transient time 0 value used  
Initial Transient Solution  
-----  

Node	Voltage
---	
in	0
out	0
v1#branch	0

  
Reference value : 0.00000e+00  
No. of Data Rows : 1512  
peak = 9.999997e-01 at= 1.500000e-08  
tp = 6.981516e-10  
tp = 6.981516e-10  
t2 = 1.103673e-10  
t3 = 2.307575e-09  
tr = 2.197208e-09  
ngspice 1 -> []

Simulation Result

From simulation results,  $tp = 0.6901$  ns and  $tr = 2.19$  ns .

So, We can observe that both the results are same and accurate by choosing those R and C values.

5) b) Considering a non-ideal step input with  $10 \text{ ps} < tr_{in} < 10 \text{ ns}$  and simulating the circuit

Netlist file:


- Varying rise time in input signal and do simulation.

```
I**Propagation delay*
V1 in 0 PULSE(0 1 0 3e-9 0) ** changing tr in the given range
R1 in out 1k
C1 out 0 1p
.tran 0.01ns 15n

.control
run
*plot V(out) V(in)
meas tran peak MAX V(out)
let vp = peak/
meas tran Tp find time when V(out)=vp cross=1
print Tp
let v2 = 0.1*peak
let v3 = 0.9*peak
meas tran T2 find time when V(out)=v2
meas tran T3 find time when V(out)=v3
let tr= T3-T2
print tr
wrdata p1.data Tp tr
.endc
.end

Saving file "/home/siva... Plain Text ▾ Tab Width: 8 ▾ Ln 2, Col 62 ▾ INS
```

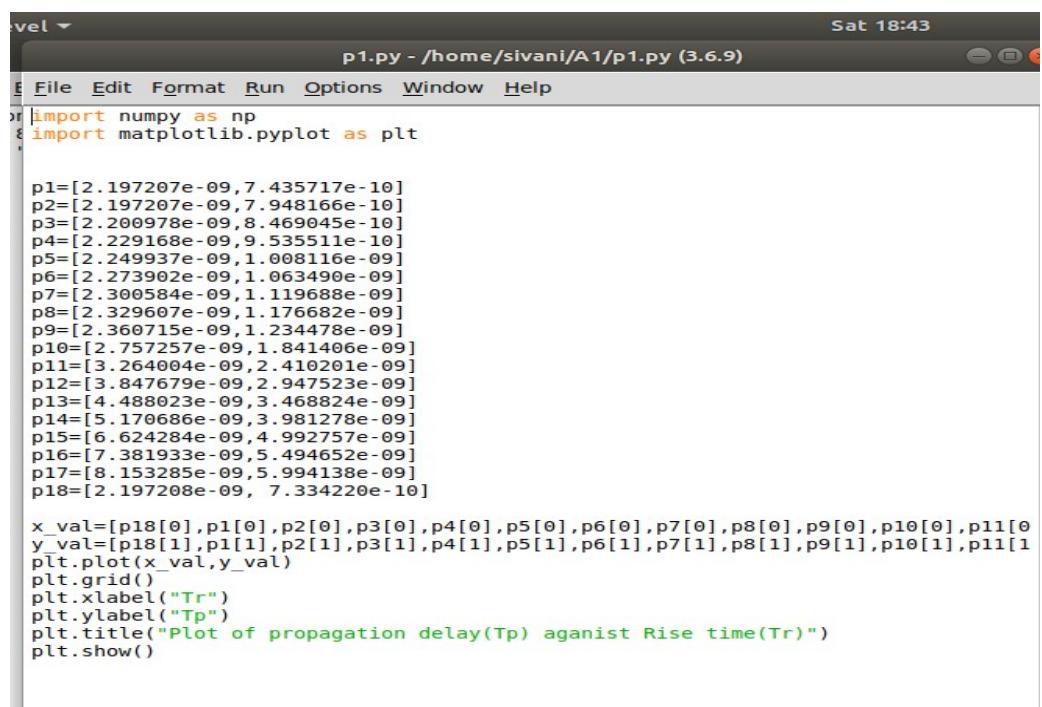Noting the points  $T_p$  and  $T_r$  and plotting in python yields a plot as shown in Fig -1.



$1e-9$  Plot of propagation delay( $T_p$ ) against Rise time( $T_r$ )


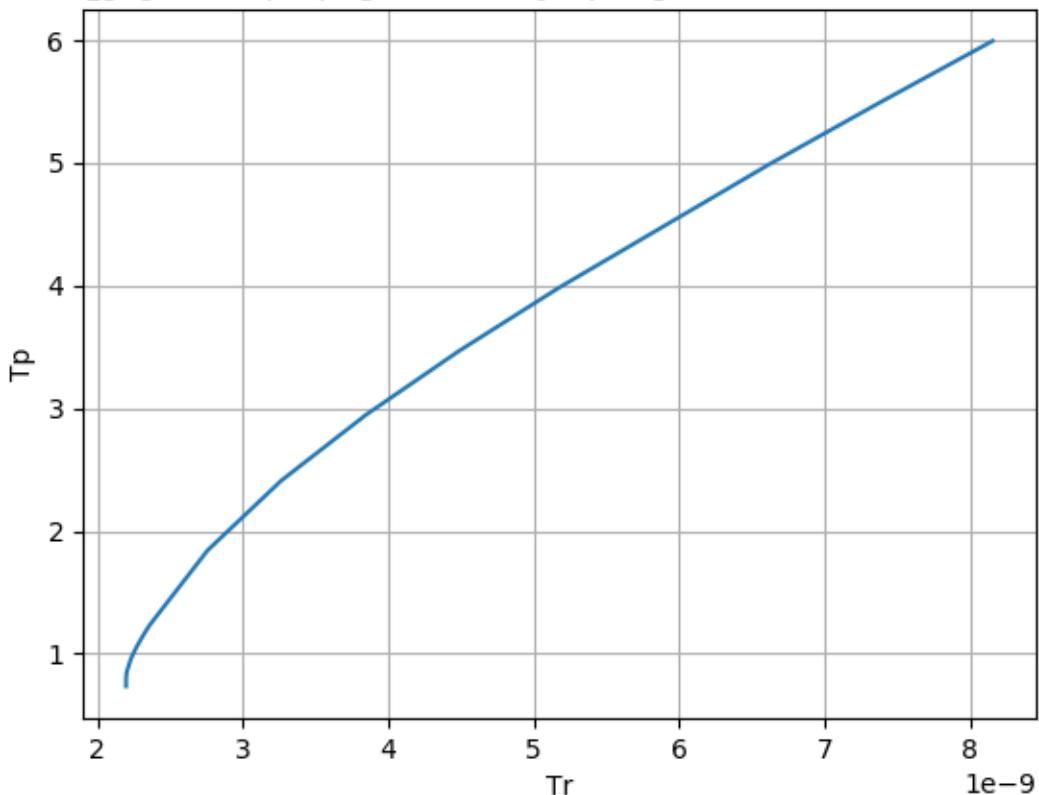


Fig - 1

5) c)

considering a non-ideal step input as,

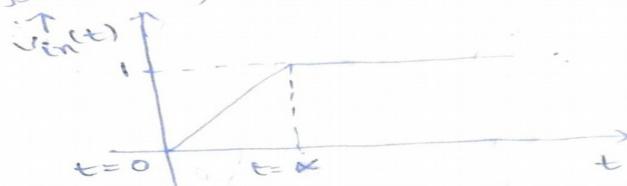

$$\therefore V_{in(t)} = \begin{cases} 0, & t \leq \alpha \\ 1, & t > \alpha \end{cases}$$

$$\therefore \frac{dV_{in(t)}}{dt} = \begin{cases} 1/\alpha, & t < \alpha \\ 0, & t > \alpha \end{cases}$$

$$\therefore \frac{dV_{in(t)}}{dt} = \frac{d}{dt}(IR + \frac{I\tau}{C})$$

$$\therefore \frac{dV_{in}}{dt} = \frac{I}{C} + R \cdot \frac{dI}{dt}$$

For  $t < \alpha$ ,

$$\frac{1}{\alpha} = \frac{I}{C} + R \cdot \frac{dI}{dt}$$

$$\Rightarrow I - \frac{C}{\alpha} = -Rc \frac{dI}{dt}$$

$$\therefore \frac{dt}{-Rc} = \frac{dI}{I - C/\alpha}$$

$$\text{At } t=0, V_{in}=0 \Rightarrow I=0$$

$$\int_{t=0}^{t=t} \frac{dt}{-Rc} = \int_{I=0}^{\frac{dI}{I - C/\alpha}}$$

$$\Rightarrow -\frac{t}{RC} = \ln \left( \frac{I - I_0/\alpha}{I_0/\alpha} \right)$$

$$\therefore I = \frac{c}{\alpha} (1 - e^{-t/RC}) \quad \text{for } t < \alpha$$

For  $t > \alpha$ ,

$$0 = \frac{I}{c} + R \cdot \frac{dI}{dt}$$

$$\int_{I_0}^I \frac{dI}{I} = \int_0^t \frac{1}{RC} dt$$

$$I_0 e^{\frac{-t}{RC}} = e^{-t/RC} \cdot e^{\alpha/RC}$$

At  $t = \alpha$ ,

$$I = I_0 = \frac{c}{\alpha} (1 - e^{-\alpha/RC})$$


For  $V_{in}$ ,  $t_r = 0.8\alpha$  as it linearly takes time  $\alpha$  to raise from '0' to 100% to 90%. So, time taking from 90% to 100% is  $0.9\alpha - 0.8\alpha = 0.1\alpha$

$$\& t_p = 0.5\alpha$$

solving for  $V_{out}$ ,

$$V_{in} - \frac{dV_o}{dt} RC - V_o = 0$$
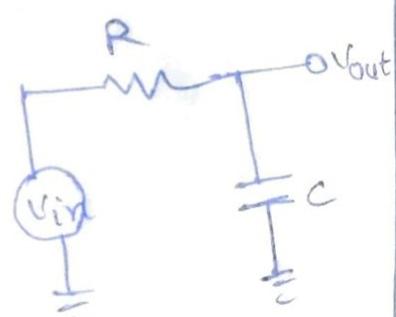
$$\frac{dV_o}{dt} = \frac{V_{in}}{RC} + \frac{V_o}{RC}$$



$$\frac{dV_0}{dt} = \frac{1}{RC} t + \frac{V_0}{RC} \quad (\text{for } t \leq \alpha)$$

For case-1:-

Solving this equation we get,

$$V_{\text{out}} = V_0 = \frac{t - RC(1 - e^{-t/RC})}{\alpha} \quad (t \leq \alpha)$$

Further,  $\alpha = 1$

~~$$\frac{dV_0}{dt} = \frac{1}{RC} t + \frac{V_0}{RC}$$~~

For case-2:-

$$V_{\text{out}} = V_0 = 1 - \frac{RC}{\alpha} (1 - e^{-\alpha/RC}) (e^{-\frac{(t-\alpha)}{RC}})$$

So, propagation delay in both cases will be as -

$$\text{In case-1: } t_p = RC \ln \left( \frac{2RC}{\alpha} (e^{\alpha/RC} - 1) \right)$$

$$\text{In case-2: } t_p = \frac{\alpha}{2} + RC (1 - e^{-tp/RC})$$

This is an implicit function so can't be solved just we can say that it is increasing function

