

# ASSIGNMENT-2

- D.Lakshmi Sivani

EE18BTECH11012

## 1)Mofset Resistance

Taking  $W/L=240/180$  and simulating the Mosfet ,

- a) For NMOS , considering  $V_{dd}=1.8V$  and initial voltage across capacitor as 1.8V.

Netlist file:

```
*Title:Q1a- NMOS Resistance

.include TSMC180.lib
.model nch_tt nmos

*Netlist


M1 ds gs 0 0 nch_tt W=0.24u L=0.18u
Vdd gs 0 DC 1.8
C1 c1 0 1pF
V2 c1 ds DC 0

.IC V(C1)=1.8
.tran 0.0005u 50u
.control

run
plot i(V2) vs V(ds)
let Req = V(ds)/i(V2)
meas tran t2 find time when v(c1)=0.9
meas tran ravg AVG Req from=0 to=t2
plot v(c1)
plot Req vs V(ds)

.endc
.end
```

## Simulation result:

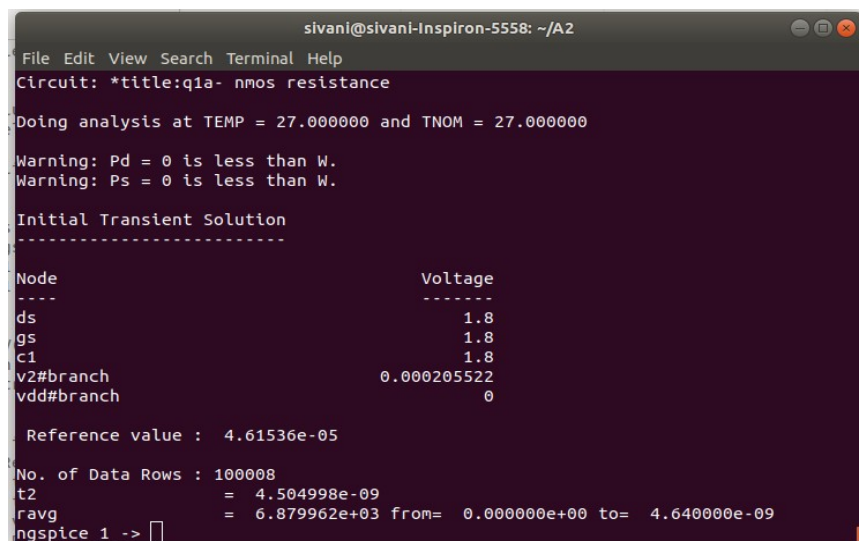

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
Circuit: *title:q1a- nmos resistance

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

Initial Transient Solution
-----
Node                Voltage
-----
ds                   1.8
gs                   1.8
c1                   1.8
v2#branch            0.000205522
vdd#branch            0

Reference value : 4.61536e-05

No. of Data Rows : 100008
t2                 = 4.504998e-09
ravg                = 6.879962e+03 from= 0.000000e+00 to= 4.640000e-09
ngspice 1 -> █
```

So, We will get Req at Vdd=1.8V as 6.879kΩ.

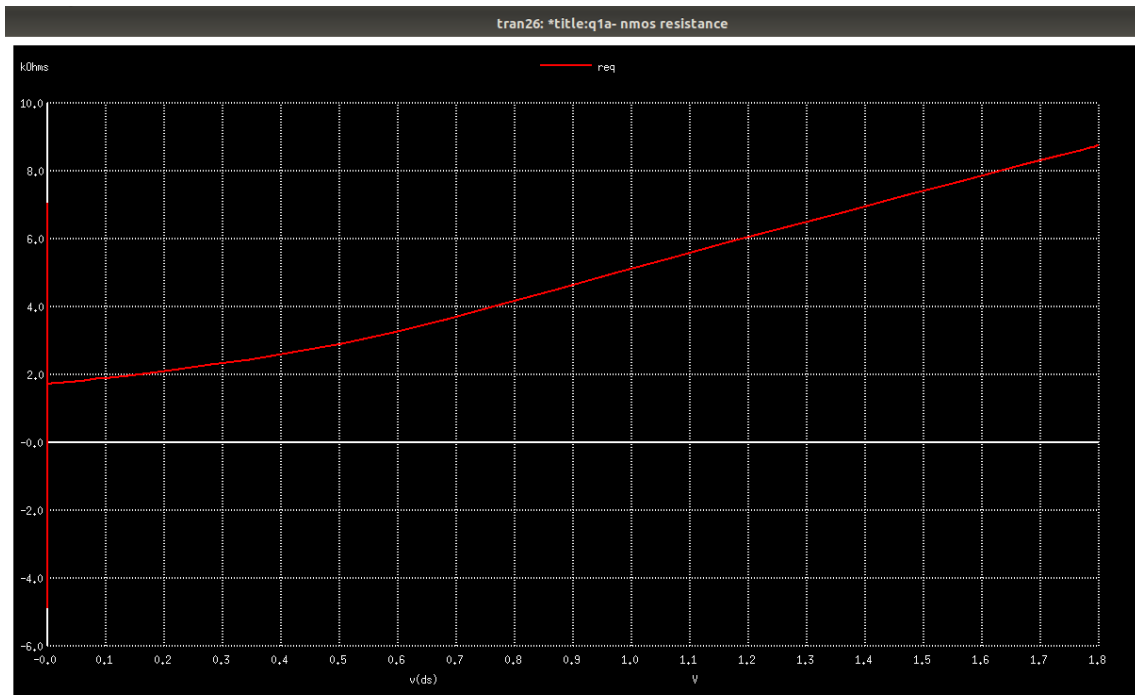


Fig-1:  $R$  Vs  $V_{dd}$  Graph(at  $V_{dd}=1.8V$ )

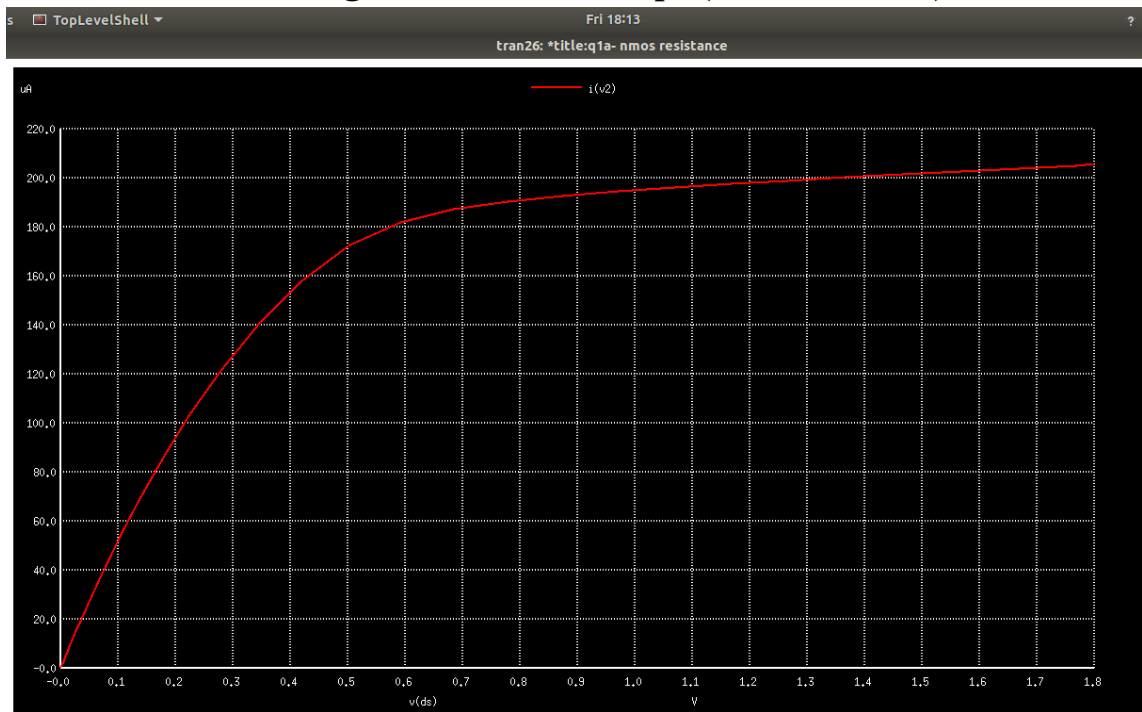


Fig -2:  $I_d$  Vs  $V_{ds}$  graph of NMOS

Similarly for PMOS simulation results are

## Netlist file:

```
*Title:Q1a- PMOS Resistance

.include TSMC180.lib
.model pch_tt pmos

*Netlist

M1 ds gs 0 0 pch_tt W=0.24u L=0.18u
Vdd gs 0 DC -1.8
C1 c1 0 1pF
V2 c1 ds DC 0

.IC V(C1)=-1.8
.tran 0.0005u 50u
.control

run
plot i(V2) vs V(ds)
let Req = V(ds)/i(V2)
meas tran t2 find time when v(c1)=-0.9
meas tran ravg AVG Req from=0 to=t2
plot v(c1)
plot Req vs V(ds)

.endc
.end
```

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
unrecognized parameter (xl) - ignored
unrecognized parameter (xw) - ignored
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000


Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

Initial Transient Solution
-----
Node              Voltage
-----
ds                 -1.8
gs                 -1.8
c1                 -1.8
v2#branch          -8.61958e-05
vdd#branch         0


Reference value : 4.84216e-05

No. of Data Rows : 100008
t2                = 1.104266e-08
ravg              = 1.645679e+04 from= 0.000000e+00 to= 1.114000e-08
ngspice 1 -> [ ]
```

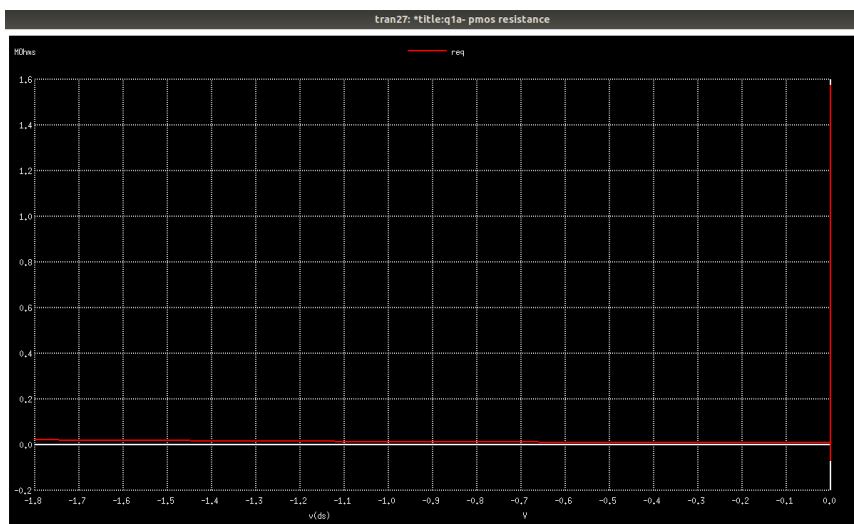So, We will get Req at Vdd=1.8V as 16.45k $\Omega$ .



R Vs Vdd Graph for pmos(at Vdd=1.8V)

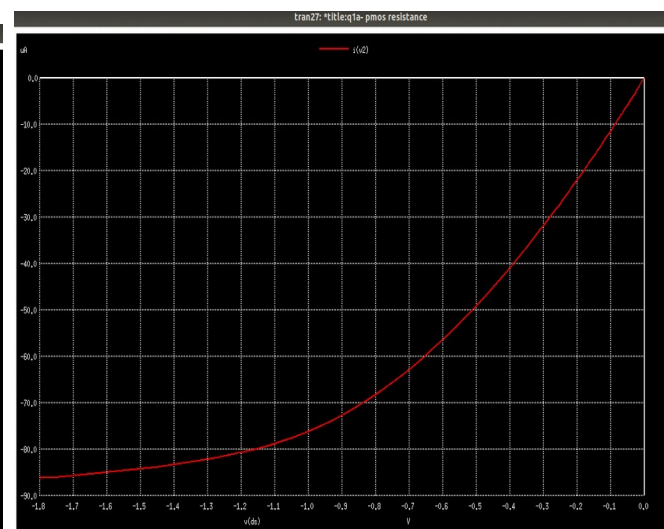

Id Vs Vdd Graph for pmos

## b) Req for different Vdds in nmos and pmos

For NMOS:  
Netlist file:

```
*Title:Q1b- NMOS Resistance with varying Vdd

.include TSMC180.lib
.model nch_tt nmos

*Netlist

M1 ds gs 0 0 nch_tt W=0.24u L=0.18u
Vdd gs 0 DC 0.6
C1 c1 0 1pF
V2 c1 ds DC 0

.IC V(C1)=0.6
.tran 0.0005u 50u
.control

run
plot i(V2) vs V(ds)
let Req = V(ds)/i(V2)
meas tran t2 find time when v(c1)=0.3
meas tran ravg AVG Req from=0 to=t2
plot V(c1)
plot Req vs V(ds)

.endc
.end
```

For Vdd=1.8V:

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
Circuit: *title:q1a- nmos resistance

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

Initial Transient Solution
-----
Node                                Voltage
----                                -
ds                                  1.8
gs                                  1.8
c1                                  1.8
v2#branch                          0.000205522
vdd#branch                          0

Reference value : 4.61536e-05

No. of Data Rows : 100008
t2                  = 4.504998e-09
ravg                = 6.879962e+03 from= 0.000000e+00 to= 4.640000e-09
ngspice 1 -> [ ]
```

So, When Vdd=1.8V, Req=6.879kΩ.

For Vdd=1.5V:

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
Circuit: *title:q1b- nmos resistance with varying vdd

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

Initial Transient Solution
-----
Node                                Voltage
----                                -
ds                                  1.5
gs                                  1.5
c1                                  1.5
v2#branch                          0.00015317
vdd#branch                          0

Reference value : 4.97041e-05

No. of Data Rows : 100008
t2                  = 5.050958e-09
ravg                = 7.708582e+03 from= 0.000000e+00 to= 5.140000e-09
ngspice 1 -> [ ]
```

So, When  $V_{dd}=1.5V$ ,  $R_{eq}=7.7k\Omega$ .

For  $V_{dd}=1.2V$ :

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
Circuit: *title:q1b- nmos resistance with varying vdd
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.
Initial Transient Solution
-----
Node          Voltage
-----
ds            1.2
gs            1.2
c1            1.2
v2#branch     9.96922e-05
vdd#branch    0
Reference value : 4.89281e-05
No. of Data Rows : 100008
t2              = 6.238649e-09
ravg            = 9.325816e+03 from= 0.000000e+00 to= 6.640000e-09
ngspice 1 ->
```

So, When  $V_{dd}=1.2V$ ,  $R_{eq}=9.325k\Omega$ .

For  $V_{dd}=0.9V$ :

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
Circuit: *title:q1b- nmos resistance with varying vdd
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.
Initial Transient Solution
-----
Node          Voltage
-----
ds            0.9
gs            0.9
c1            0.9
v2#branch     4.83046e-05
vdd#branch    0
Reference value : 4.78156e-05
No. of Data Rows : 100008
t2              = 9.751521e-09
ravg            = 1.452800e+04 from= 0.000000e+00 to= 1.014000e-08
ngspice 1 ->
```

So, When  $V_{dd}=0.9V$ ,  $R_{eq}=14.528k\Omega$ .

For  $V_{dd}=0.6V$ :

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
Circuit: *title:q1b- nmos resistance with varying vdd
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.
Initial Transient Solution
-----
Node          Voltage
-----
ds            0.6
gs            0.6
c1            0.6
v2#branch     7.50728e-06
vdd#branch    0
Reference value : 4.69621e-05
No. of Data Rows : 100008
t2              = 4.328849e-08
ravg            = 6.395063e+04 from= 0.000000e+00 to= 4.364000e-08
ngspice 1 ->
```

So, When  $V_{dd}=0.6V$ ,  $R_{eq}=63.95k\Omega$ .

Similarly,  
For PMOS  
Netlist file:

```
*Title:Q1b- PMOS Resistance with varying Vdd

.include TSMC180.lib
.model pch_tt pmos

*Netlist

M1 ds gs 0 0 pch_tt W=0.24u L=0.18u
Vdd gs 0 DC -0.6
C1 c1 0 1pF
V2 c1 ds DC 0

.IC V(C1)=-0.6
.tran 0.0005u 50u
.control

run
plot i(V2) vs V(ds)
let Req = V(ds)/i(V2)
meas tran t2 find time when v(c1)=-0.3
meas tran ravg AVG Req from=0 to=t2
plot v(c1)
plot Req vs V(ds)

.endc
.end
```

For Vdd=1.8V:

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
unrecognized parameter (xl) - ignored
unrecognized parameter (xw) - ignored
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

Initial Transient Solution
-----
Node                Voltage
-----
ds                  -1.8
gs                  -1.8
c1                  -1.8
v2#branch           -8.61958e-05
vdd#branch          0

Reference value : 4.84216e-05

No. of Data Rows : 100008
t2                = 1.104266e-08
ravg              = 1.645679e+04 from= 0.000000e+00 to= 1.114000e-08
ngspice 1 -> 
```

So,When Vdd=1.8V Req=16.45kΩ.

For Vdd=1.5V:

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
unrecognized parameter (xl) - ignored
unrecognized parameter (xw) - ignored
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

Initial Transient Solution
-----
Node                Voltage
-----
ds                  -1.5
gs                  -1.5
c1                  -1.5
v2#branch           -5.44996e-05
vdd#branch          0

Reference value : 4.85161e-05

No. of Data Rows : 100008
t2                = 1.454376e-08
ravg              = 2.165675e+04 from= 0.000000e+00 to= 1.464000e-08
ngspice 1 -> 
```

So,When Vdd=1.5V Req=21.656kΩ.



For Vdd=1.2V:

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
unrecognized parameter (xl) - ignored
unrecognized parameter (xw) - ignored
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

Initial Transient Solution
-----
Node                                Voltage
----                                -
ds                                  -1.2
gs                                  -1.2
c1                                  -1.2
v2#branch                          -2.90118e-05
vdd#branch                          0

Reference value : 4.85591e-05

No. of Data Rows : 100008
t2                = 2.182223e-08
ravg              = 3.237323e+04 from= 0.000000e+00 to= 2.214000e-08
ngspice 1 -> □
```

So,When Vdd=1.2V Req=32.37kΩ.

For Vdd=0.9V:

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
unrecognized parameter (xl) - ignored
unrecognized parameter (xw) - ignored
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

Initial Transient Solution
-----
Node                                Voltage
----                                -
ds                                  -0.9
gs                                  -0.9
c1                                  -0.9
v2#branch                          -1.13518e-05
vdd#branch                          0

Reference value : 4.93926e-05

No. of Data Rows : 100008
t2                = 4.171249e-08
ravg              = 6.185030e+04 from= 0.000000e+00 to= 4.214000e-08
ngspice 1 -> □
```

So,When Vdd=0.9V Req=61.85kΩ.

For Vdd=0.6V:

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
unrecognized parameter (xl) - ignored
unrecognized parameter (xw) - ignored
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

Initial Transient Solution
-----
Node                                Voltage
----                                -
ds                                  -0.6
gs                                  -0.6
c1                                  -0.6
v2#branch                          -1.86754e-06
vdd#branch                          0

Reference value : 4.96666e-05

No. of Data Rows : 100008
t2                = 1.687231e-07
ravg              = 2.503531e+05 from= 0.000000e+00 to= 1.691400e-07
ngspice 1 -> □
```

So,When Vdd=0.6V Req=250.3kΩ.

Writing these results in a table gives,

	Vdd=1.8V	Vdd=1.5V	Vdd=1.2V	Vdd=0.9V	Vdd=0.6V
NMOS(in k $\Omega$ )	6.879	7.7	9.325	14.528	63.95
PMOS(in k $\Omega$ )	16.45	21.656	32.37	61.85	250.3

## 2)Mosfet Capacitance

a) Given W/L=2.5

For Short channel NMOS(L=0.18um,W=0.45um)

Simulation results are

Netlist file:

```
*Title:Q2a-Short channel NMOS CV

.include "TSMC180.lib"
.model nch_tt nmos

*Netlist
Vgs1 n1 0 DC 2
Vgs2 T n1 DC 0 AC 1 SINE(0 0.003183 50)
M1 0 G 0 0 nch_tt W=0.45u L=10u
Vt T G DC 0

.control
run
let vgs1 = 2
while vgs1 >= -2
    alter @Vgs1 vgs1
    tran 10u 20m
    meas tran c1 FIND i(Vt) AT = 20m
    print vgs1
    plot i(Vt) xlabel "Current waveform at VCM $&vgs1"
    let vgs1 = vgs1 - 0.25
end
.endc
.end
```

Through this simulation,we will get values of C and Vgs.Then plot these points in python results in Mosfet Capacitance graph for short channel NMOS.

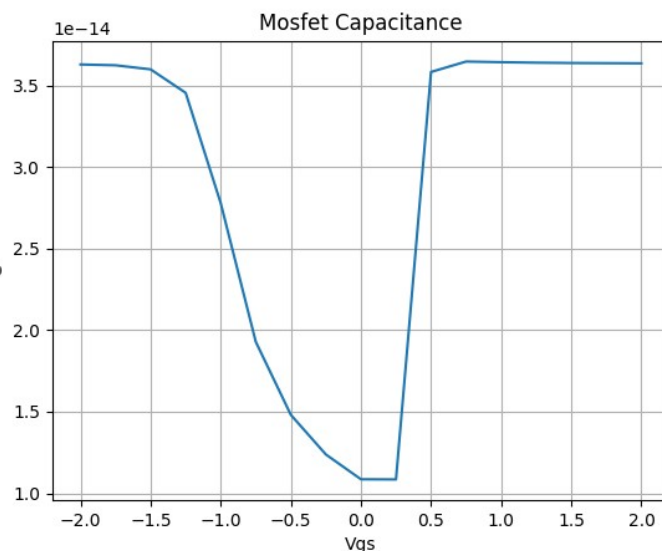


Fig-1:CV characteristics for short channel NMOS



```

File Edit Format Run Options Window Help
import numpy as np
import matplotlib.pyplot as plt

p1=[3.637e-14,2]
p2=[3.638e-14,1.75]
p3=[3.639e-14,1.5]
p4=[3.641e-14,1.25]
p5=[3.644e-14,1]
p6=[3.648e-14,0.75]
p7=[3.584e-14,0.5]
p8=[1.085e-14,0.25]
p9=[1.086e-14,0]
p10=[1.238e-14,-0.25]
p11=[1.481e-14,-0.5]
p12=[1.929e-14,-0.75]
p13=[2.779e-14,-1]
p14=[3.456e-14,-1.25]
p15=[3.6e-14,-1.5]
p16=[3.625e-14,-1.75]
p17=[3.63e-14,-2]

x_val=[p1[0],p2[0],p3[0],p4[0],p5[0],p6[0],p7[0],p8[0],p9[0],p10[0],p11[0],p12[0],p13[0],p14[0],p15[0],p16[0],p17[0]]
y_val=[p1[1],p2[1],p3[1],p4[1],p5[1],p6[1],p7[1],p8[1],p9[1],p10[1],p11[1],p12[1],p13[1],p14[1],p15[1],p16[1],p17[1]]
plt.plot(y_val,x_val)
plt.grid()
plt.xlabel("Vgs")
plt.ylabel("C")
plt.title("Mosfet Capacitance")
plt.show()

```

For Long channel NMOS(L=25um,W=10um)

Simulation results are

Netlist file:

```

*Title:Q2a-Long channel NMOS CV

.include "TSMC180.lib"
.model nch_tt nmos

*Netlist
Vgs1 n1 0 DC 2
Vgs2 T n1 DC 0 AC 1 SINE(0 0.003183 50)
M1 0 G 0 0 nch_tt W=25u L=10u
Vt T G DC 0

.control
run
let vgs1 = 2
while vgs1 >= -2
    alter @Vgs1 vgs1
    tran 10u 20m
    meas tran c1 FIND i(Vt) AT = 20m
    print vgs1
    plot i(Vt)          xlabel "Current waveform at VCM $&vgs1"
    let vgs1 = vgs1 - 0.25
end
.endc
.end

```

Through this simulation,we will get values of C and Vgs.Then plot these points in python results in Mosfet Capacitance graph for long channel NMOS.

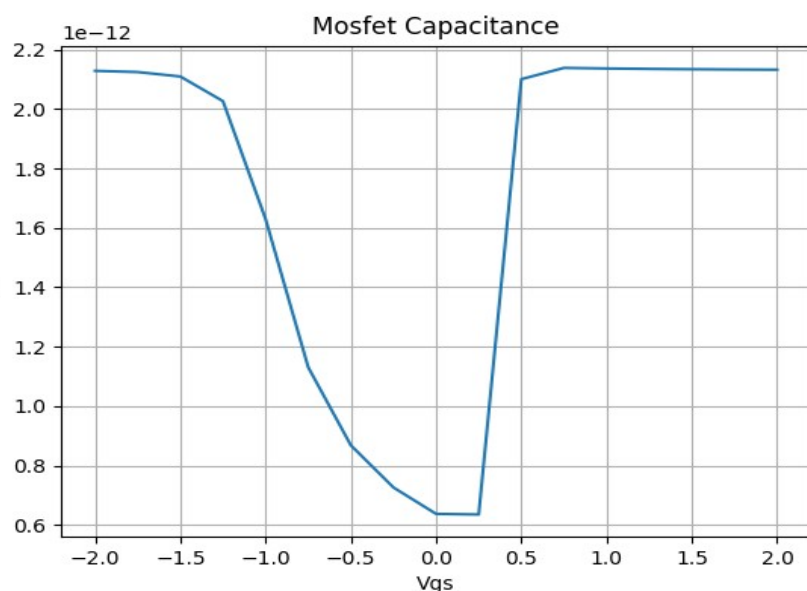


Fig-2:CV characteristics for long channel NMOS

```

import numpy as np
import matplotlib.pyplot as plt

p1=[2.13297e-12,2]
p2=[2.133627e-12,1.75]
p3=[2.134473e-12,1.5]
p4=[2.1356e-12,1.25]
p5=[2.137e-12,1]
p6=[2.139e-12,0.75]
p7=[2.101e-12,0.5]
p8=[6.35e-13,0.25]
p9=[6.37e-13,0]
p10=[7.26e-13,-0.25]
p11=[8.68e-13,-0.5]
p12=[1.131e-12,-0.75]
p13=[1.63e-12,-1]
p14=[2.027e-12,-1.25]
p15=[2.11e-12,-1.5]
p16=[2.125e-12,-1.75]
p17=[2.129e-12,-2]

x_val=[p1[0],p2[0],p3[0],p4[0],p5[0],p6[0],p7[0],p8[0],p9[0],p10[0],p11[0],p12[0],p13[0],p14[0],p15[0],p16[0],p17[0]]
y_val=[p1[1],p2[1],p3[1],p4[1],p5[1],p6[1],p7[1],p8[1],p9[1],p10[1],p11[1],p12[1],p13[1],p14[1],p15[1],p16[1],p17[1]]
plt.plot(y_val,x_val)
plt.grid()
plt.xlabel("C")
plt.ylabel("Vgs")
plt.title("Mosfet Capacitance")
plt.show()

```

## b)CV characteristics with change of frequency

For long channel nmos,

with  $f=10\text{M Hz}$

Netlist file:

```

*Title:Q2b-Long channel NMOS CV


.include "TSMC180.lib"
.model nch_tt nmos

*Netlist
Vgs1 n1 0 DC 2
Vgs2 T n1 DC 0 AC 1 SINE(0 0.159e-7 1e7)
M1 0 G 0 0 nch_tt W=25u L=10u
Vt T G DC 0

.control
run
let vgs1 = 2
while vgs1 >= -2
    alter @Vgs1 vgs1
    tran 10u 20m
    meas tran c1 FIND i(Vt) AT = 20m
    print vgs1
    plot i(Vt) xlabel "Current waveform at VCM $&vgs1"
    let vgs1 = vgs1 - 0.25
end
.endc
.end

```

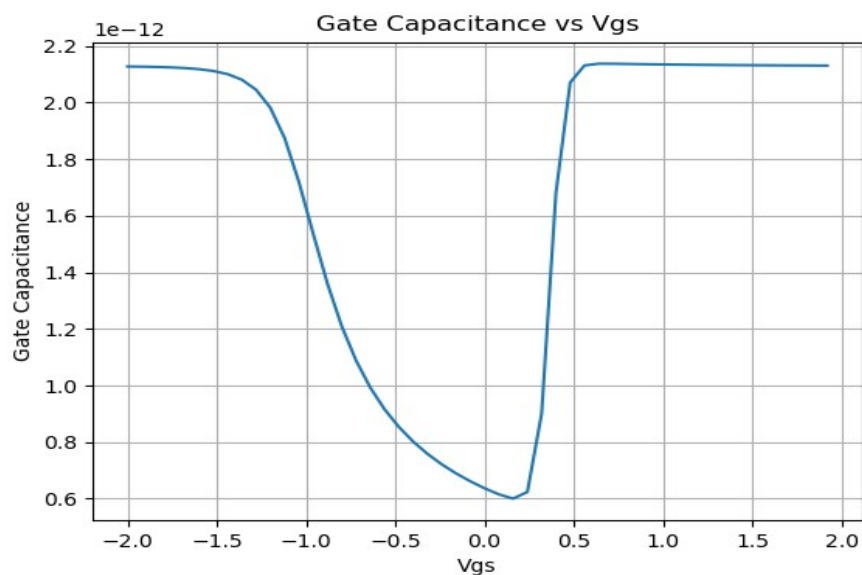Plotting these simulation points in python yields mosfet capacitance graph as



With  $f = 10\text{GHz}$ ,

Netlist file:


```
*Title:Q2b-Long channel NMOS CV

.include "TSMC180.lib"
.model nch_tt nmos

*Netlist
Vgs1 n1 0 DC 2
Vgs2 T n1 DC 0 AC 1 SINE(0 0.159e-10 10e9)
M1 0 G 0 0 nch_tt W=25u L=10u
Vt T G DC 0

.control
run
let vgs1 = 2
while vgs1 >= -2
    alter @Vgs1 vgs1
    tran 10u 20m
    meas tran c1 FIND i(Vt) AT = 20m
    print vgs1
    plot i(Vt)          xlabel "Current waveform at VCM $&vgs1"
    let vgs1 = vgs1 - 0.25
end
.endc
.end
```

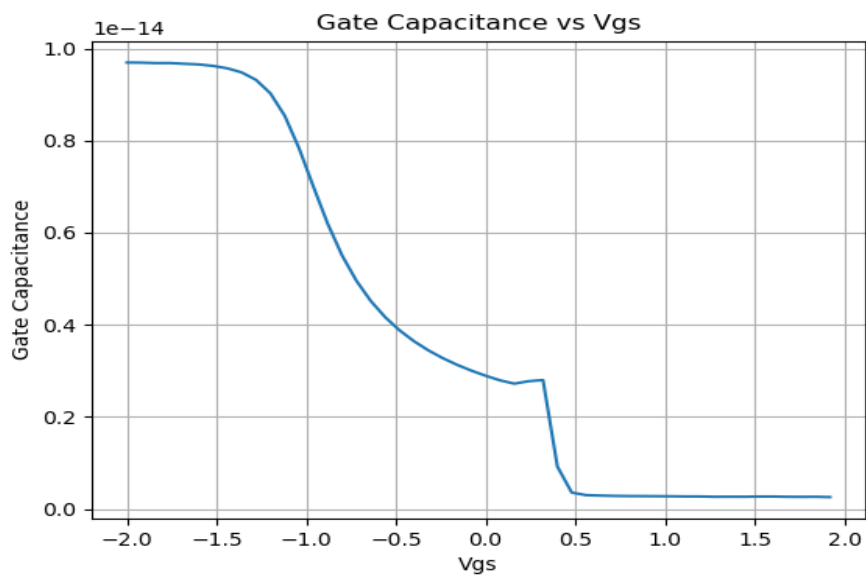Plotting these simulation points in python yields mosfet capacitance graph as



**For short channel NMOS,**

with  $f=10\text{M Hz}$ ,


Netlist file:

```
.include "TSMC180.lib"
.model nch_tt nmos

*Netlist
Vgs1 n1 0 DC 2
Vgs2 T n1 DC 0 AC 1 SINE(0 0.159e-7 1e7)
M1 0 G 0 0 nch_tt W=0.45u L=0.18u
Vt T G DC 0

.control
run
let vgs1 = 2
while vgs1 >= -2
    alter @Vgs1 vgs1
    tran 10u 20m
    meas tran c1 FIND i(Vt) AT = 20m
    print vgs1
    plot i(Vt)          xlabel "Current waveform at VCM $&vgs1"
    let vgs1 = vgs1 - 0.25
end
.endc
.end
```

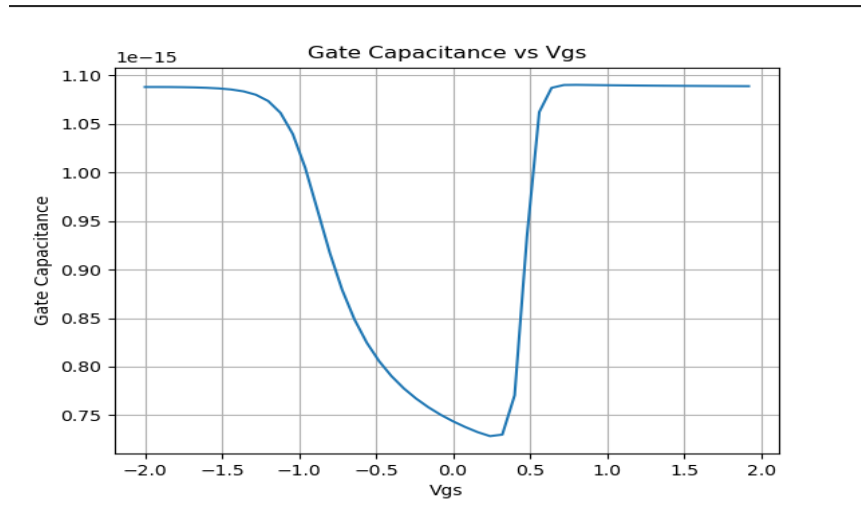Plotting these simulation points in python yields mosfet capacitance graph as



With  $f = 10\text{GHz}$ ,

Netlist file:


```
*Title:Q2b-Short channel NMOS CV

.include "TSMC180.lib"
.model nch_tt nmos

*Netlist
Vgs1 n1 0 DC 2
Vgs2 T n1 DC 0 AC 1 SINE(0 0.159e-10 10e9)
M1 0 G 0 0 nch_tt W=0.45u L=0.18u
Vt T G DC 0

.control
run
let vgs1 = 2
while vgs1 >= -2
    alter @Vgs1 vgs1
    tran 10u 20m
    meas tran c1 FIND i(Vt) AT = 20m
    print vgs1
    plot i(Vt)          xlabel "Current waveform at VCM $&vgs1"
    let vgs1 = vgs1 - 0.25
end
.endc
.end
```

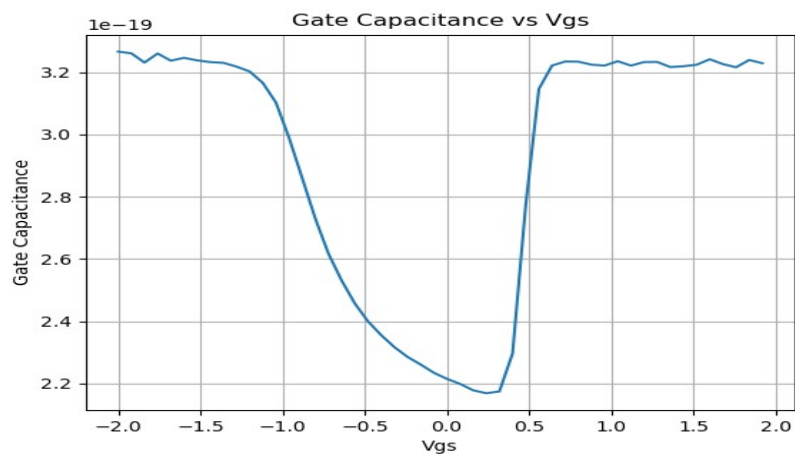Plotting these simulation points in python yields mosfet capacitance graph as



## 5)NMOS Inverter

Results obtained analytically in question-4 are:

$V_{OH}=2.5V$                        $V_{iL}=0.3837 V$       Noise margin low= $0.3597 V$

$V_{OL}=24.08mV$                        $V_{iH}=0.684 V$       Noise margin high= $1.816 V$

$V_M=0.6403 V$                       Peak gain= $-10.399$

Now we shall compare these with simulations

### a) Simulating the given circuit


#### Netlist File:

```
*Title:Q5a-Gain of NMOS Inverter
.include TSMC180.lib
.model nch_tt nmos

*Netlist
Vdd 1 0 2.5
Rl 1 out 75k
Vin in 0 1
M1 out in 0 0 nch_tt W=0.54u L=0.18u

.control
dc Vin 0 3 0.01
let gain = deriv(V(out))
plot gain
meas dc Vol find V(out) at=2.5 cross=1
meas dc Voh find V(out) at=0
meas dc Vm find V(out) when V(out)=V(in)
meas dc Vil when gain=-1 cross=1
meas dc Vih when gain=-1 cross=2
let NMh = Voh-Vih
let NML = Vil-Vol
print NMh
print NML
meas dc peakgain MIN gain
plot V(out)

.endc
.end
```

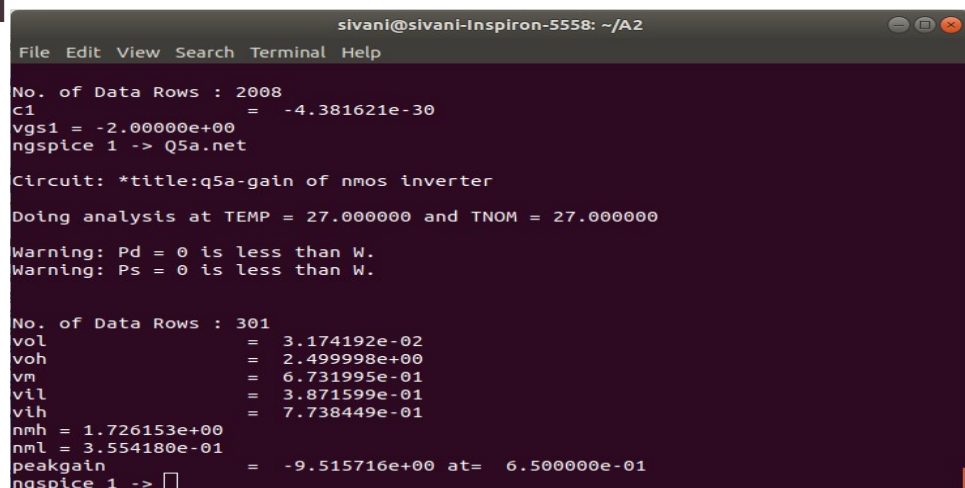

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help

No. of Data Rows : 2008
c1 = -4.381621e-30
vgs1 = -2.000000e+00
ngspice 1 -> Q5a.net

Circuit: *title:q5a-gain of nmos inverter
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

No. of Data Rows : 301
vol = 3.174192e-02
voh = 2.499998e+00
vm = 6.731995e-01
vil = 3.871599e-01
vih = 7.738449e-01
nmh = 1.726153e+00
nml = 3.554180e-01
peakgain = -9.515716e+00 at= 6.500000e-01
ngspice 1 -> □
```

From these simulations we obtained,

$V_{OH}=2.499V$                        $V_{iL}=0.3871 V$       Noise margin low= $0.3554 V$

$V_{OL}=31.7mV$                        $V_{iH}=0.7738 V$       Noise margin high= $1.726 V$

$V_M=0.673 V$                       Peak gain=  $-9.515$

So, These simulation results are similar to analytical values.

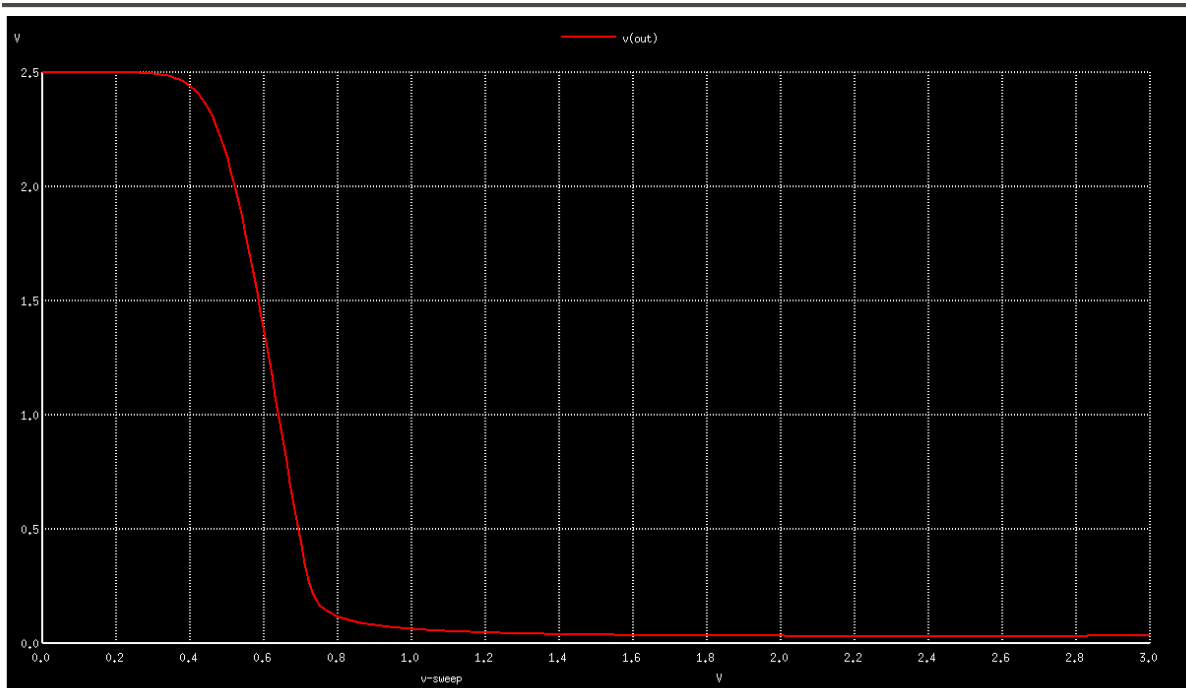


Fig:Graph of  $V_{out}$

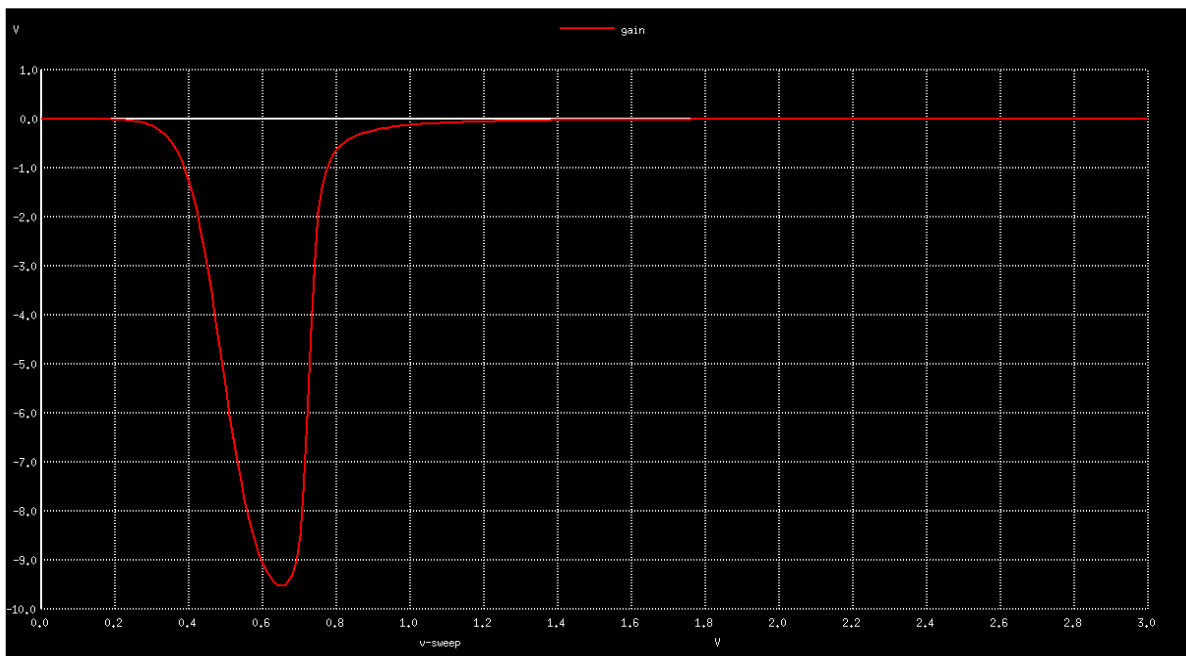


Fig:Plot of Gain of Inverter

## b) Impact of load resistance on threshold( $V_M$ ) and peak-gain of Inverter.

Let us consider  
 $R_L = 6k\Omega$  and  
 simulate

Netlist file:

```
.include TSMC180.lib
.model nch_tt nmos

*Netlist
Vdd 1 0 2.5
RL 1 out 6k
Vin in 0 1
M1 out in 0 0 nch_tt W=0.54u L=0.18u

.control
dc Vin 0 3 0.01
let gain = deriv(V(out))
plot gain
meas dc Vol find V(out) at=2.5 cross=1
meas dc Voh find V(out) at=0
meas dc Vm find V(out) when V(out)=V(in)
meas dc Vil when gain=-1 cross=1
meas dc Vih when gain=-1 cross=2
let NMh = Voh-Vih
let NML = Vil-Vol
print NMh
print NML
meas dc peakgain MIN gain
plot V(out)
.endc
.end
```



```

sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
Error(parse.c--checkvalid): vil: no such vector.
Error(parse.c--checkvalid): nmh: no such vector.
Error(parse.c--checkvalid): nml: no such vector.
peakgain      = -3.092402e-01 at= 1.220000e+00
ngspice 1 -> Q5a.net

Circuit: *title:q5b-gain of nmos inverter
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

No. of Data Rows : 301
vol      = 4.285629e-01
voh      = 2.500000e+00
vm       = 1.282686e+00
vil      = 5.615429e-01
vih      = 1.716112e+00
nmh      = 7.838880e-01
nml      = 1.329800e-01
peakgain = -1.680549e+00 at= 1.150000e+00
ngspice 1 -> 

```

Let us consider  $R_L=1G \Omega$  and simulate

Netlist file:

```

*Title:Q5b-Gain of NMOS Inverter
.include TSMC180.lib
.model nch_tt nmos

*Netlist
Vdd 1 0 2.5
RL 1 out 1e9
Vin in 0 1
M1 out in 0 0 nch_tt W=0.54u L=0.18u

.control
dc Vin 0 3 0.01
let gain = deriv(V(out))
plot gain
meas dc Vol find V(out) at=2.5 cross=1
meas dc Voh find V(out) at=0
meas dc Vm find V(out) when V(out)=V(in)
meas dc Vil when gain=-1 cross=1
meas dc Vih when gain=-1 cross=2
let NMH = Voh-Vih
let NML = Vil-Vol
print NMH
print NML
meas dc peakgain MIN gain
plot V(out)
.endc
.end

```

```

sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
vih      = 1.716112e+00
nmh      = 7.838880e-01
nml      = 1.329800e-01
peakgain = -1.680549e+00 at= 1.150000e+00
ngspice 1 -> Q5a.net

Circuit: *title:q5b-gain of nmos inverter
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.

No. of Data Rows : 301
vol      = 2.363255e-06
voh      = 2.472216e+00
vm       = 2.298608e-01
vil      = 1.381283e-02
vih      = 2.597311e-01
nmh      = 2.212485e+00
nml      = 1.381047e-02
peakgain = -1.884902e+01 at= 2.100000e-01
ngspice 1 -> 

```

So, from above considered simulations of load resistance range we can conclude that Threshold( $V_M$ ) decreases with increase in load resistance where as Peak gain increases with increase in load resistance.

## c) Simulating the circuit

### Netlist file:

```
File: /home/sivani/A2/Q5c.net Page 1 of 1

*Title:Q5c-VTC of NMOS Inverter

.include TSMC180.lib
.model nch_tt nmos

*netlist

Vdd 1 0 2.5
R1 1 out 75k
C1 out 0 3p
Vin in 0 PULSE(0 2.5 0 0 0 2u 4u)

M1 out in 0 0 nch_tt W=0.54u L=0.18u


.control
tran 0.01u 10u 0u
plot V(out) V(in)
meas tran Voutpeak MAX V(out)
meas tran Vinpeak MAX V(in)
let v1 = Voutpeak/2
let v2 = 0.1*Voutpeak
let v3 = 0.9*Voutpeak
let v4 = Vinpeak/2
meas tran T1 when V(in)=v2 cross=1
meas tran T2 when V(in)=v3 cross=1
meas tran T3 when V(in)=v2 cross=2
meas tran T4 when V(in)=v3 cross=2
meas tran T5 when V(in)=v1 cross=1
meas tran T6 when V(out)=v4 cross=1
meas tran T7 when V(in)=v1 cross=2
meas tran T8 when V(out)=v4 cross=2
let Tpl = T5-T6
let Tph = T7-T8
let Tr = T2-T1
let Tf = T3-T4
print Tr
print Tf
print (Tpl+Tph)/2
.endc
.end
```

```
sivani@sivani-Inspiron-5558: ~/A2
File Edit View Search Terminal Help
-----
1 2.5
out 2.5
in 0
vin#branch 0
vdd#branch -2.82365e-11

No. of Data Rows : 1050
voutpeak = 2.500021e+00 at= 8.000000e-10
vinpeak = 2.500000e+00 at= 1.000000e-05
t1 = 1.000008e-09
t2 = 9.000076e-09
t3 = 2.019000e-06
t4 = 2.011000e-06
t5 = 5.000044e-09
t6 = 1.282583e-08
t7 = 2.015000e-06
t8 = 2.169378e-06
tr = 8.000068e-09
tf = 8.000000e-09
(tpl+tp)/2 = -8.11019e-08
ngspice 1 ->
```

Here  $t_r$  and  $t_f$  both are equal to  $8 \times 10^{-9}$  approximately. So, both rise and fall time are equal.  $T_p = 8.11 \times 10^{-8}$

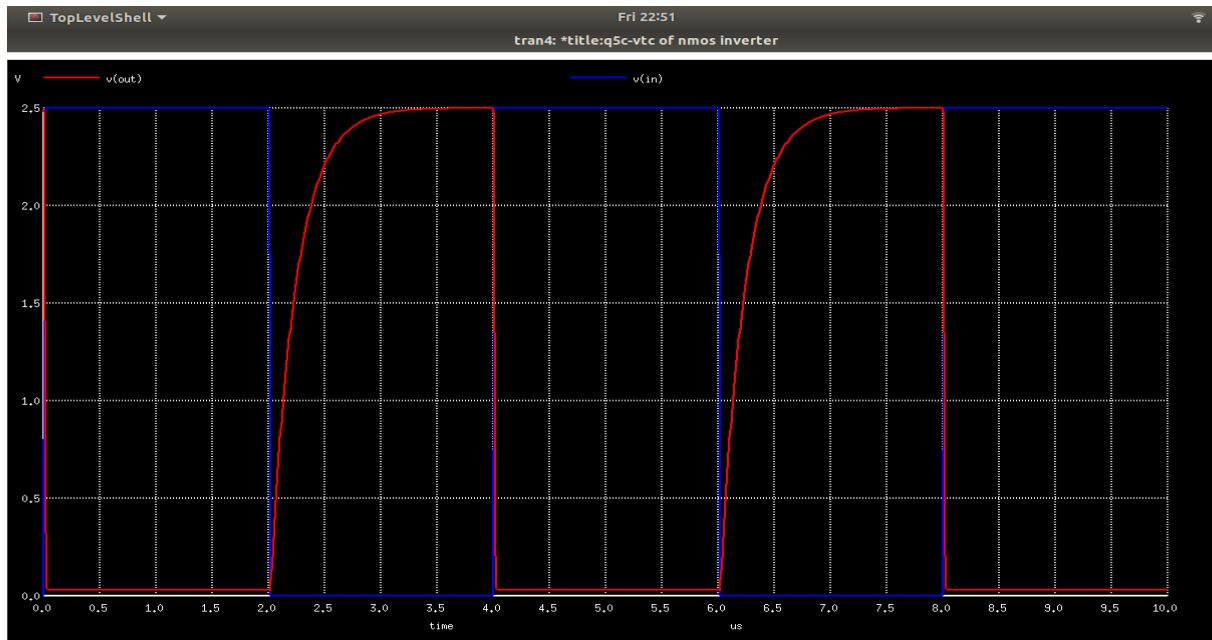- We know that maximum operating frequency depends on  $T_p$ .  $T_p$  is inversely proportional to  $f$  (since  $R_{on}$  increases with decrease in  $W/L$ ). So, Maximum frequency is also inversely proportional to  $W/L$ . The maximum frequency depends on  $W, L$  of mosfet (geometric parameters).



Vin-Vout Graph